



COMPUTER ORGANISATION (TỔ CHỨC MÁY TÍNH)

Processor: Datapath

Acknowledgement

- The contents of these slides have origin from School of Computing, National University of Singapore.
- We greatly appreciate support from Mr. Aaron Tan Tuck Choy for kindly sharing these materials.

Policies for students

- These contents are only used for students PERSONALLY.
- Students are NOT allowed to modify or deliver these contents to anywhere or anyone for any purpose.

Road Map: Part II

Performance


Assembly
Language

**Processor:
Datapath**

Processor:
Control

Pipelining

Cache

 

■ Processor Datapath

- ❑ Generic Execution Stages
- ❑ MIPS Execution Stages
- ❑ Constructing Datapath

Building a Processor: Datapath & Control


- Two major components for a processor:
- **Datapath**
 - Collection of components that process data
 - Performs the arithmetic, logical and memory operations
- **Control**
 - Tells the datapath, memory, and I/O devices **what to do** according to program instructions

MIPS Processor: Implementation

- Simplest possible implementation of a subset of the core MIPS ISA:
 - **Arithmetic and Logical operations**
 - `add, sub, and, or, addi, andi, ori, slt`
 - **Data transfer instructions**
 - `lw, sw`
 - **Branches**
 - `beq, bne`
- Shift instructions (`sll, srl`) and J-type instructions (`j`) will not be discussed here
 - Left as exercises 😊

Recap: Instruction Execution Cycle

Important!

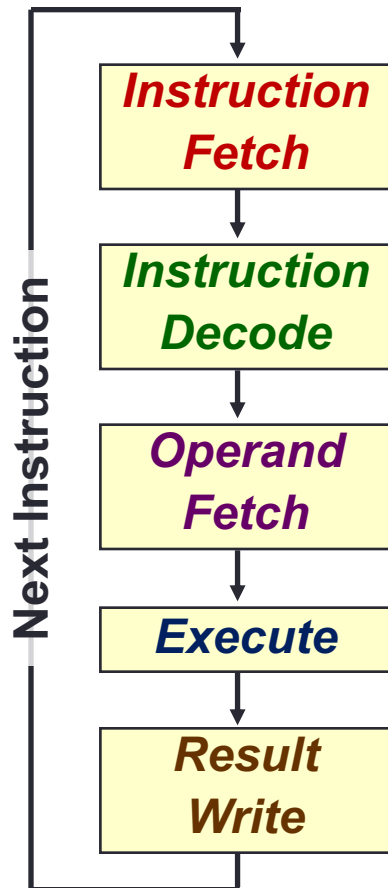

- **Fetch:**
 - Get instruction from memory
 - Address is in **P**rogram **C**ounter (PC) Register
- **Decode:**
 - Find out the operation required
- **Operand Fetch:**
 - Get operand(s) needed for operation
- **Execute:**
 - Perform the required operation
- **Result Write (WriteBack):**
 - Store the result of the operation

MIPS Instruction Executions

- Show the actual steps for 3 representative MIPS instructions
- Fetch and Decode stages not shown:
 - The standard steps are performed

	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20(\$1)</code>	<code>beq \$1, \$2, ofst</code>
Fetch	<i>standard</i>	<i>standard</i>	<i>standard</i>
Decode			
Operand Fetch	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i>
Execute	$Result = opr1 + opr2$	<ul style="list-style-type: none"> ○ $MemAddr = opr1 + opr2$ ○ Use <i>MemAddr</i> to read data from memory 	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) \text{ or } (PC+4) + ofst$
Result Write	<i>Result</i> stored in \$3	<i>Memory data</i> stored in \$3	PC = <i>Target</i>

- **opr** = Operand
- **MemAddr** = Memory Address

- **ofst** = offset

5-STAGE MIPS EXECUTION

- Design changes:
 - Merge *Decode* and *Operand Fetch* – Decode is simple for MIPS
 - Split *Execute* into **ALU** (Calculation) and **Memory Access**

	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20(\$1)</code>	<code>beq \$1, \$2, ofst</code>
Fetch	Read inst. at [PC]	Read inst. at [PC]	Read inst. at [PC]
Decode & Operand Fetch	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Read [\$2] as <i>opr2</i>
ALU	$Result = opr1 + opr2$	$MemAddr = opr1 + opr2$	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) \text{ or } (PC+4) + ofst$
Memory Access		Use <i>MemAddr</i> to read data from memory	
Result Write	<i>Result</i> stored in \$3	<i>Memory data</i> stored in \$3	PC = <i>Target</i>

Let's Build a MIPS Processor!

- What we are going to do:
 - Look at each stage closely, figure out the requirements and processes
 - Sketch a high level block diagram, then zoom in for each elements
 - With the simple starting design, check whether different type of instructions can be handled:
 - Add modifications when needed
- ➔ Study the design from the viewpoint of a designer, instead of a “tourist” 😊

Fetch Stage: Requirements

- Instruction **Fetch Stage**:

1. Use the **Program Counter (PC)** to fetch the instruction from **memory**

- PC is implemented as a special register in the processor


2. **Increment** the PC by 4 to get the address of the next instruction:

- How do we know the next instruction is at PC+4?
- Note the exception when branch/jump instruction is executed

- Output to the next stage (**Decode**):


- The instruction to be executed

Fetch Stage: Block Diagram

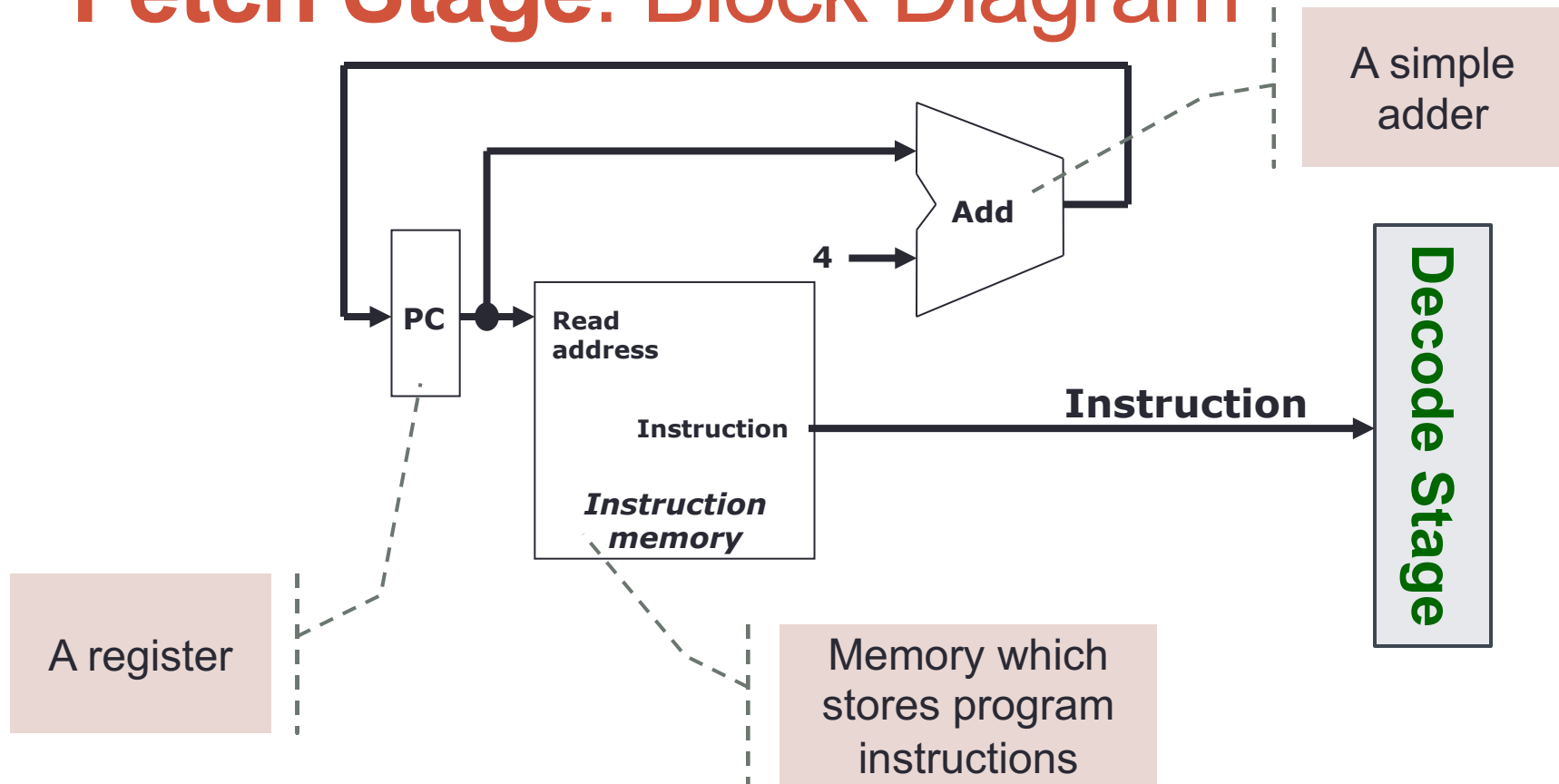

Element: Instruction Memory

 - Storage element for the instructions
 - Recall: **sequential circuit**
 - Has an internal state that stores information
 - Clock signal is assumed and not shown
- Supply instructions given the address
 - Given instruction address M as input, the memory outputs the content at address M
 - Conceptual diagram of the memory layout is given on the right →



Memory	

2048	add \$3, \$1, \$2
2052	sll \$4, \$3, 2
2056	andi \$1, \$4, 0xF
.....

Element: Adder


- Combinational logic to implement the addition of two numbers

- **Inputs:**

- Two 32-bit numbers **A**, **B**

- **Output:**


- Sum of the input numbers, **A + B**

 

- Just a 32-bit version of the adder discussed in first part of the course 😊

The Idea of Clocking

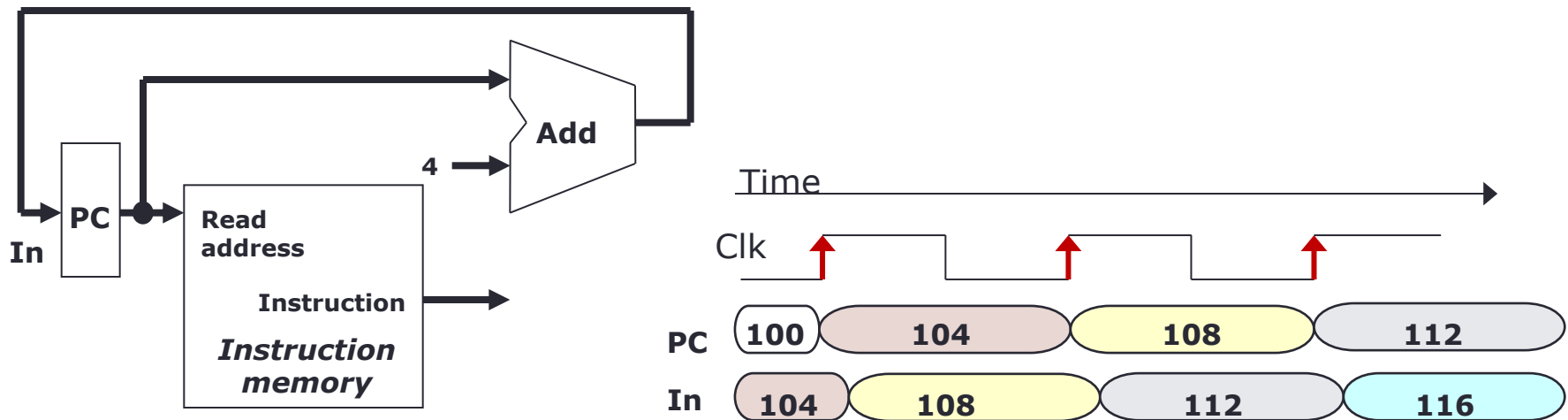
- It seems that we are reading and updating the PC at the same time:
 - How can it work properly?
- **Magic of clock:**
 - PC is read during the first half of the clock period and it is updated with PC+4 at the **next rising clock edge**



Decode Stage: Requirement


- Instruction **Decode Stage**:
 - Gather data from the instruction fields:
 1. Read the **opcode** to determine instruction type and field lengths
 2. Read data from all necessary registers
 - Can be two (e.g. **add**), one (e.g. **addi**) or zero (e.g. **j**)
- Input from previous stage (**Fetch**):
 - Instruction to be executed
- Output to the next stage (**ALU**):
 - Operation and the necessary operands

Decode Stage: Block Diagram

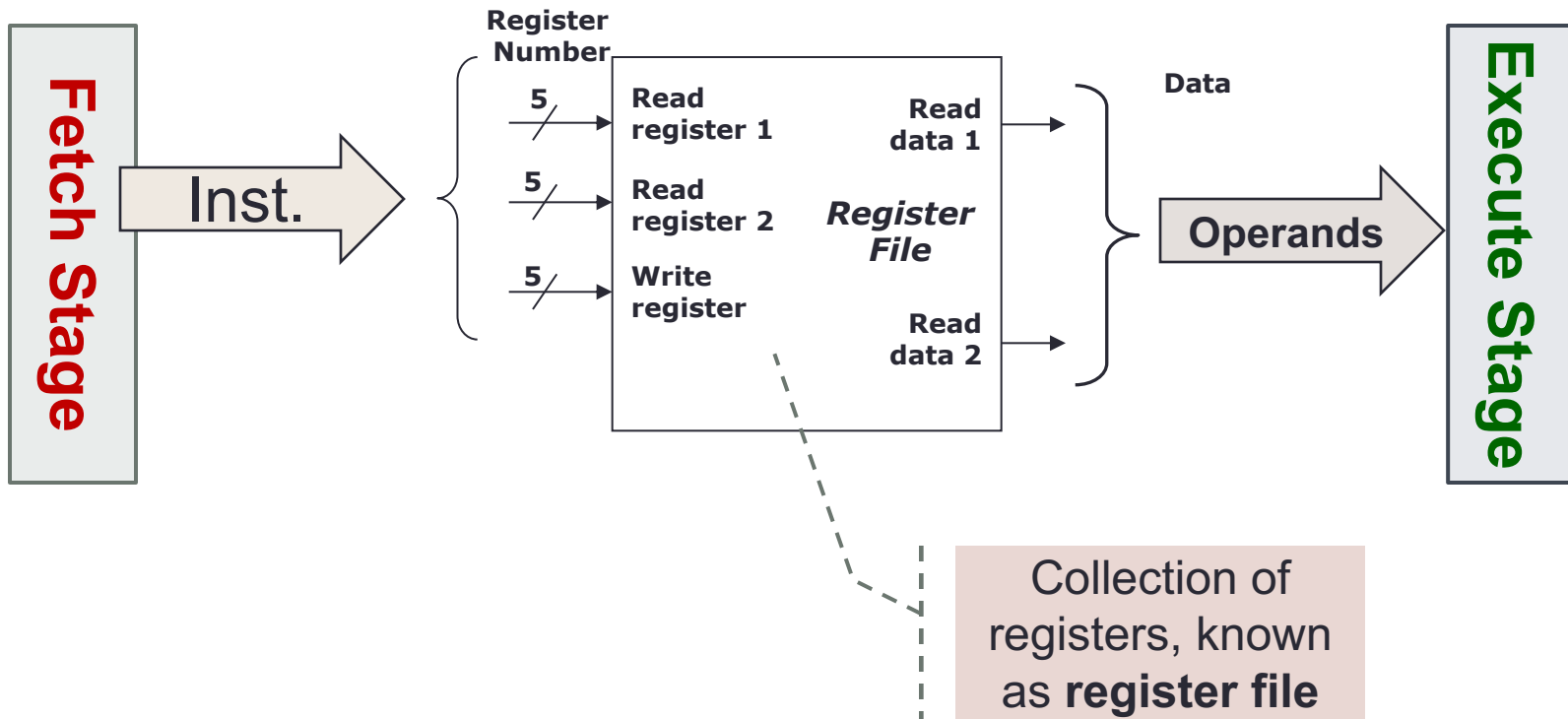


Element: Register File

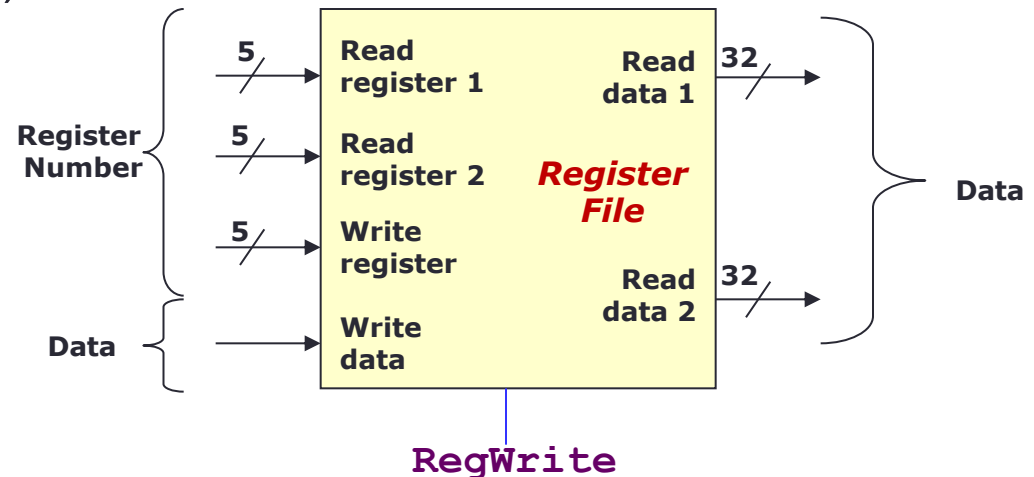- A collection of 32 registers:
 - Each is 32-bit wide and can be read/written by specifying register number
 - Read at most two registers per instruction
 - Write at most one register per instruction
- **RegWrite** is a control signal to indicate:
 - Writing of register
 - 1(True) = Write, 0 (False) = No Write




Decode Stage: R-Type Instruction

add \$8, \$9, \$10

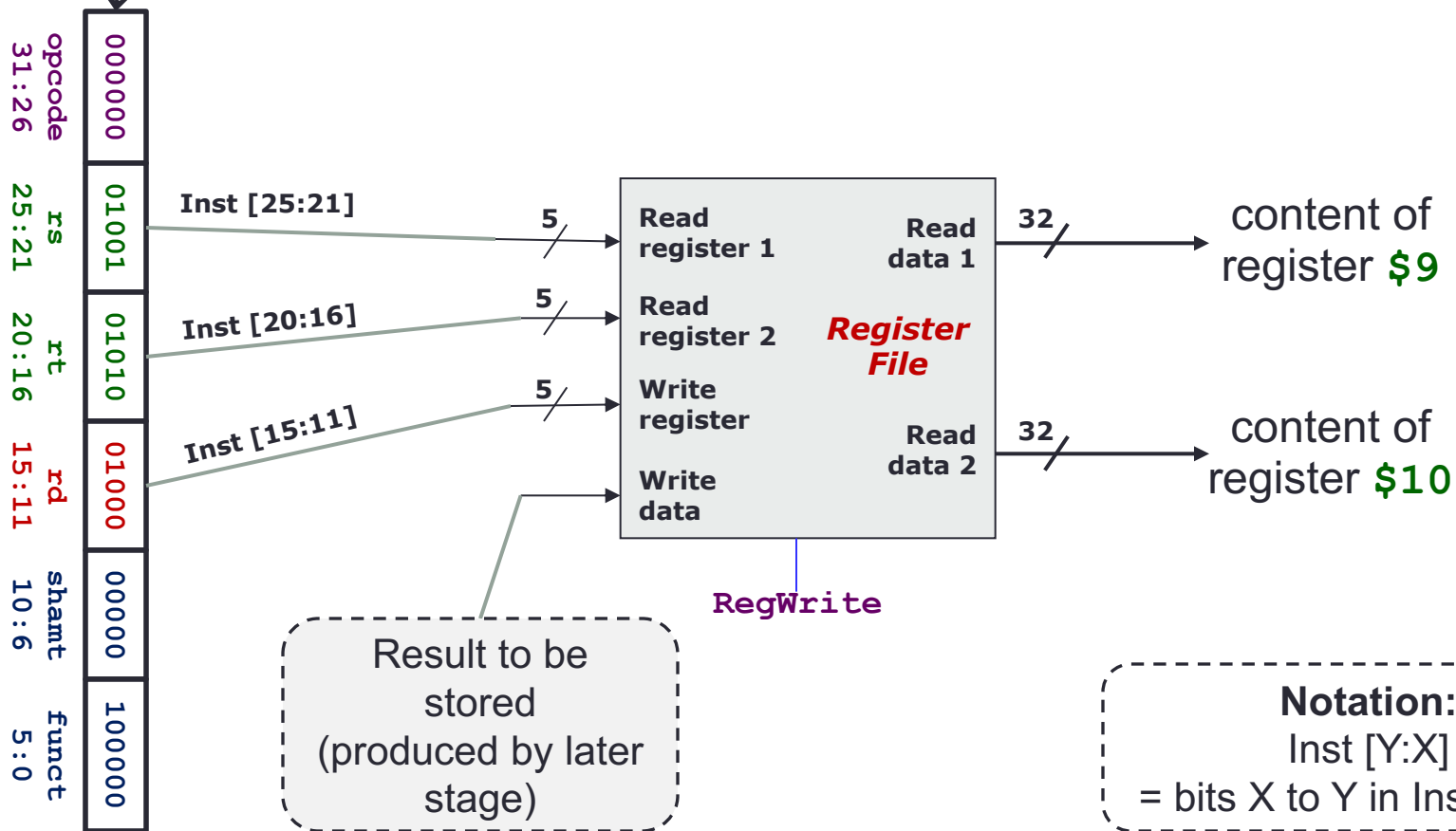

Decode Stage: I-Type Instruction

addi \$21, \$22, -50

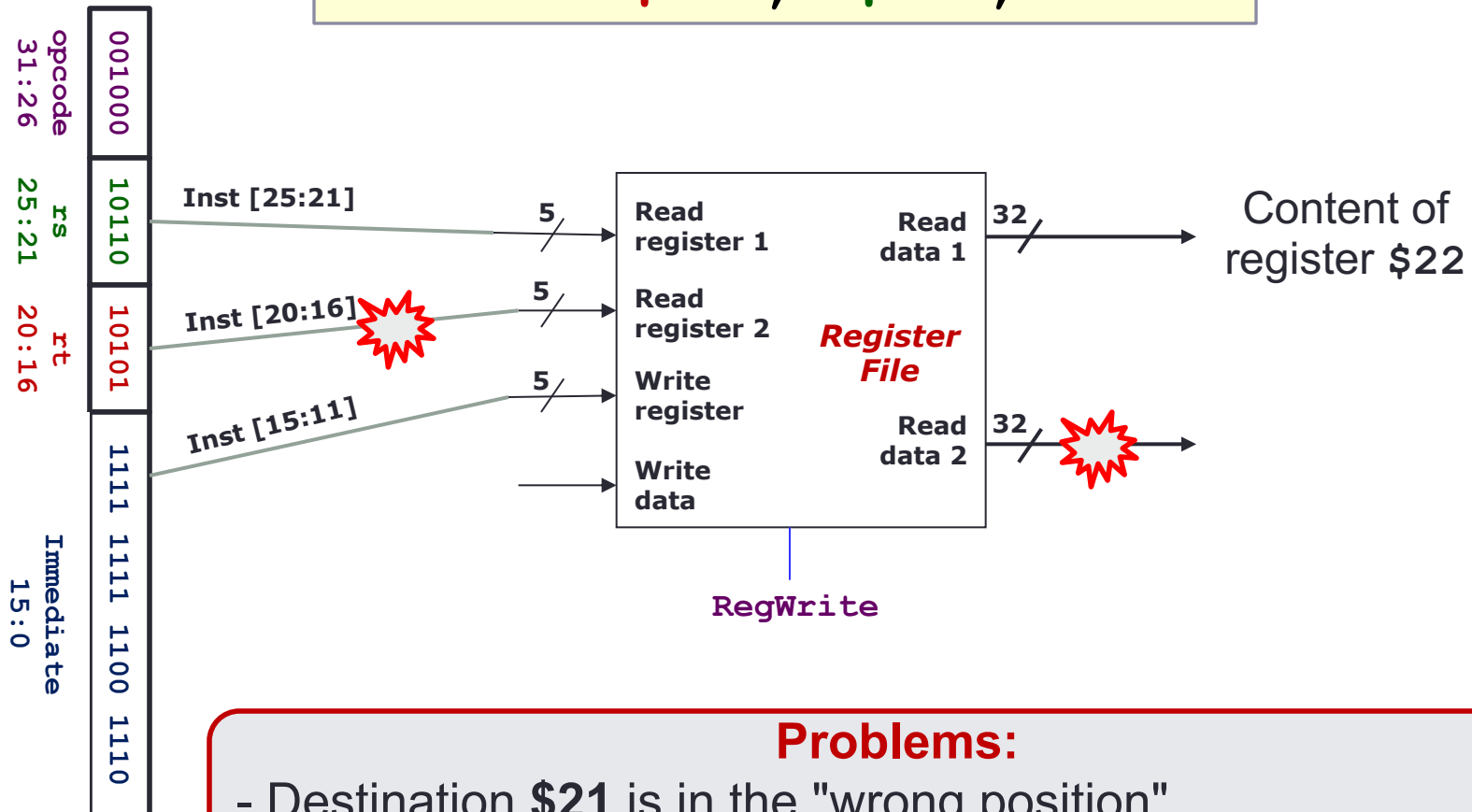


Problems:

- Destination **\$21** is in the "wrong position"
- **Read Data 2** is an immediate value, not from register

Decode Stage: Choice in Destination

addi \$21, \$22, -50

 

Solution (Wr. Reg. No.):
Use a **multiplexer** to choose the correct write register number based on instruction type

Recap: Multiplexer

- **Function:**

- Selects one input from multiple input lines

- **Inputs:**


- n lines of same width

- **Control:**

- m bits where $n = 2^m$

- **Output:**


- Select i^{th} input line if control= i

 

Control=0 \rightarrow select in_0
Control=3 \rightarrow select in_3


Decode Stage: Choice in Data 2

addi \$21, \$22, -50

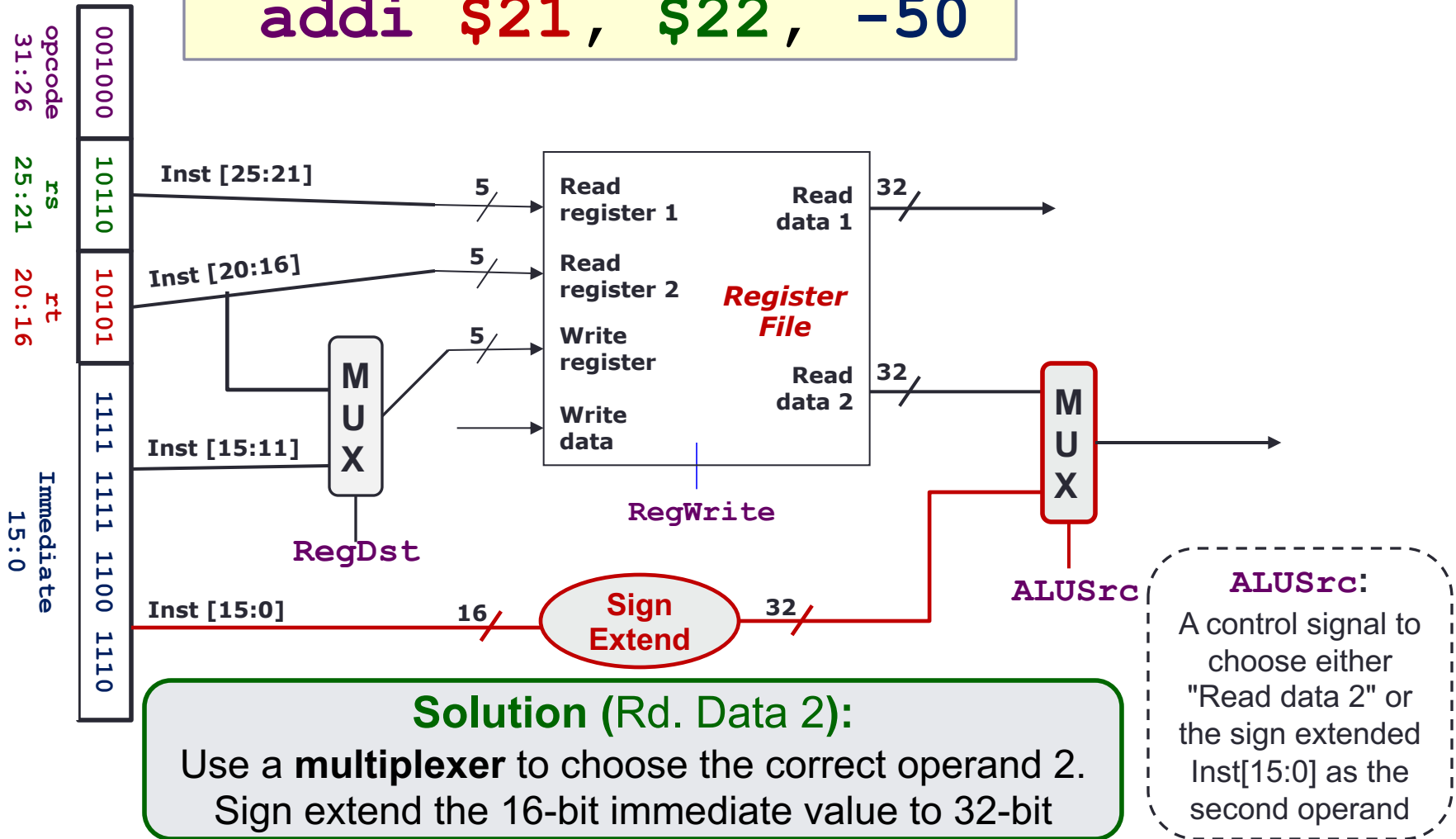


Decode Stage: Load Word Instruction

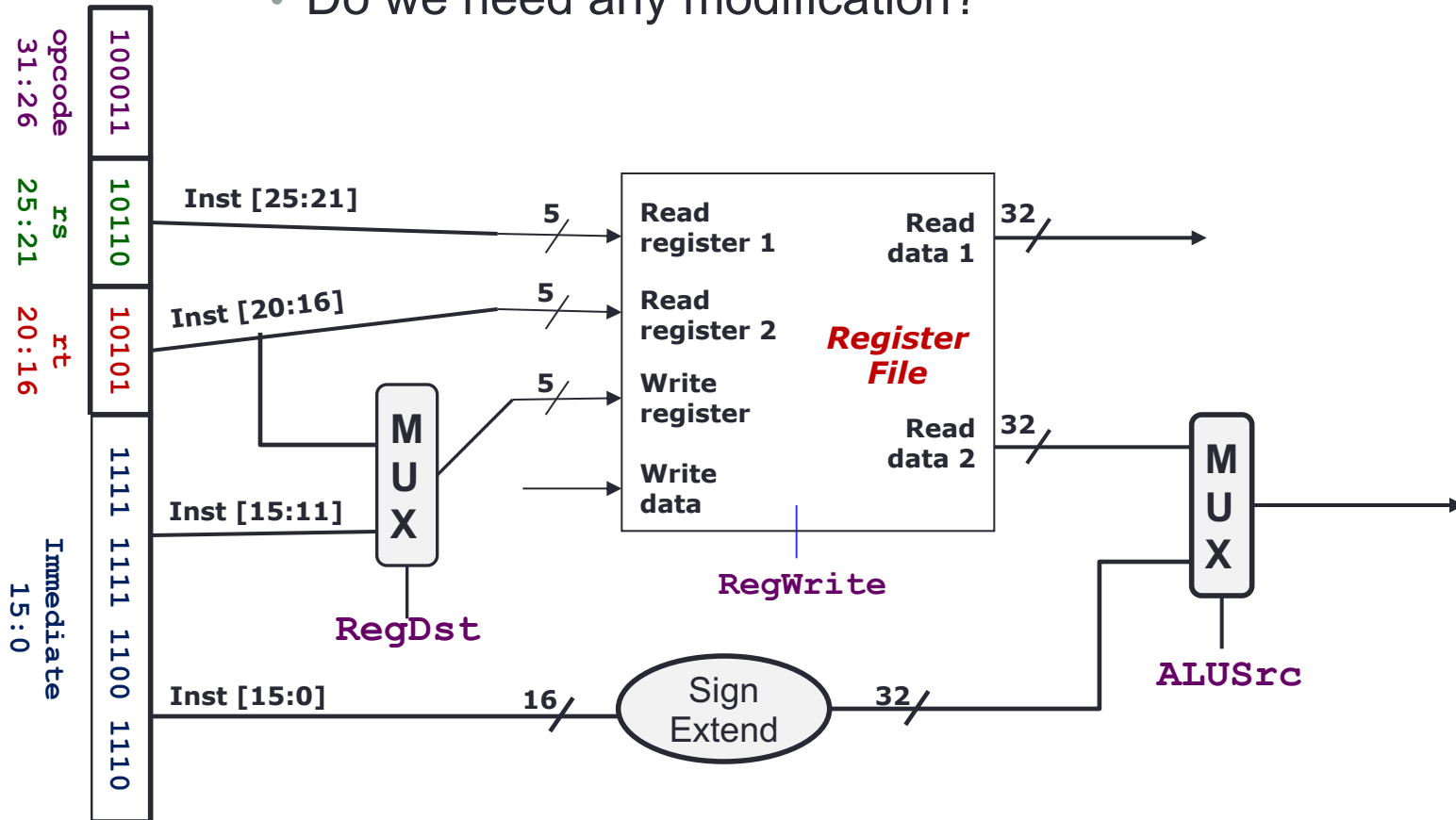- Try it out: "**lw** **\$21**, -50 (**\$22**)"
- Do we need any modification?




Decode Stage: Branch Instruction

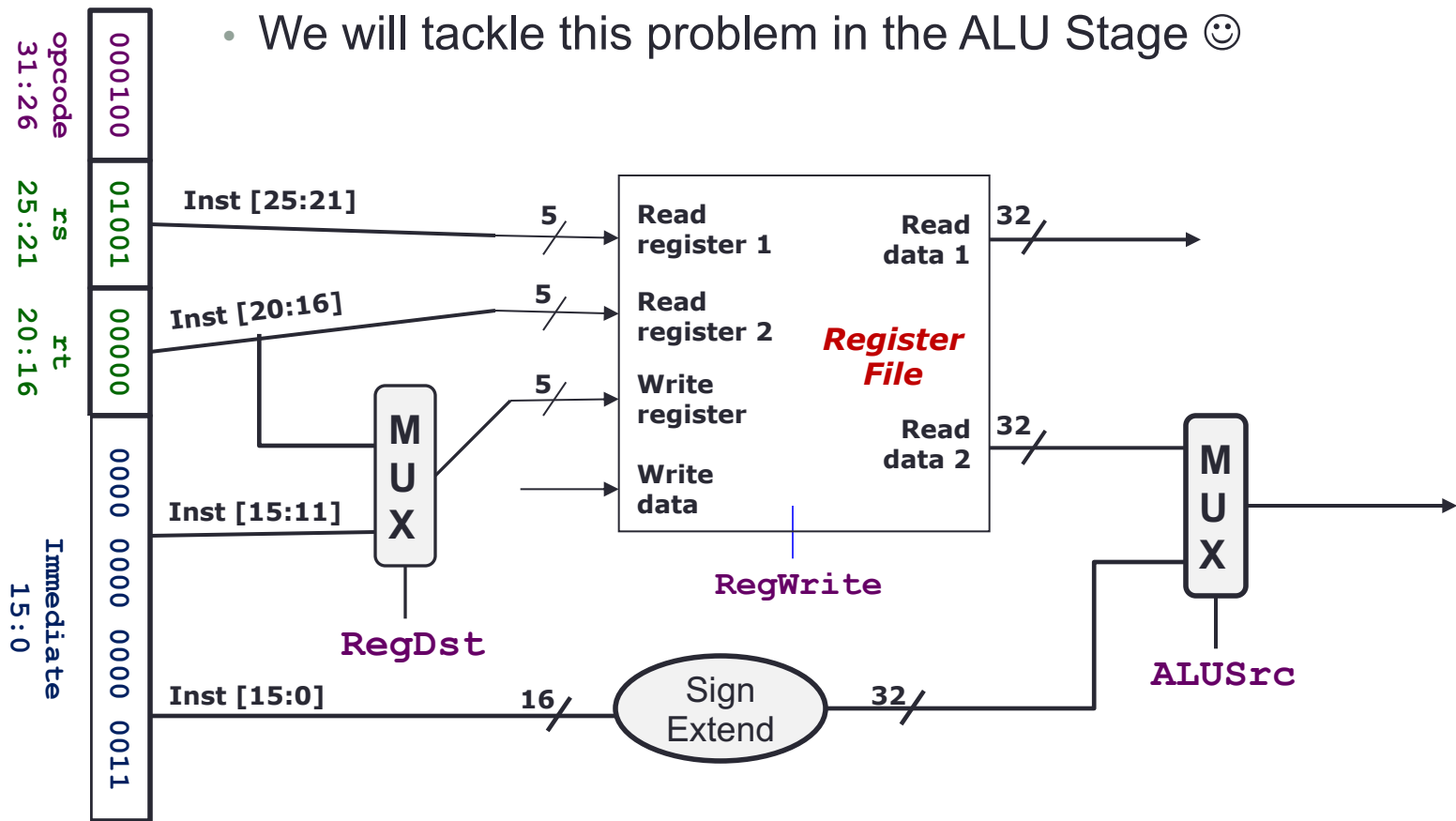- Example: "**beq** \$9, \$0, 3"
 - Need to calculate branch outcome and target at the same time!
 - We will tackle this problem in the ALU Stage ☺




Decode Stage: Summary

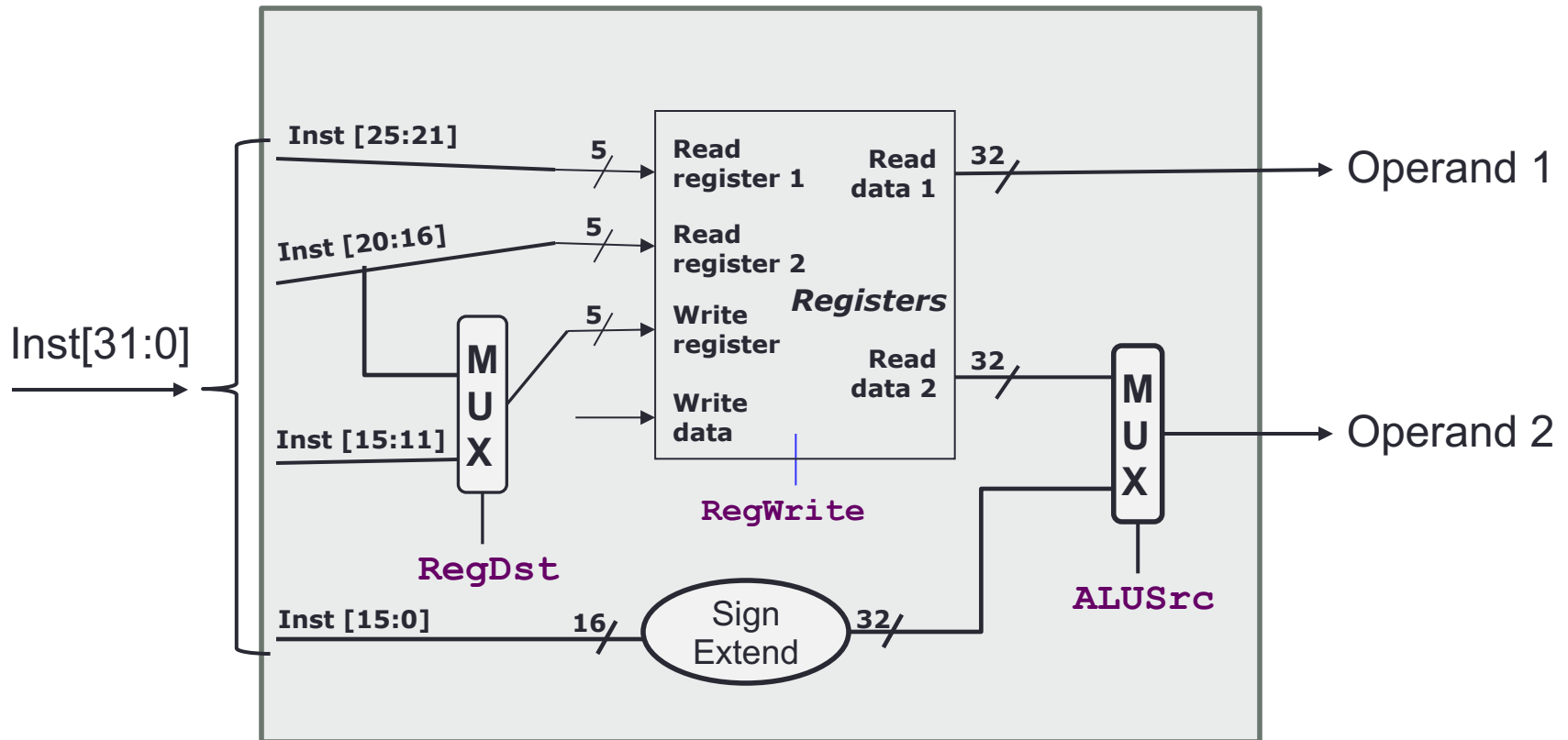

ALU Stage: Requirement

- Instruction **ALU Stage**:
 - ALU = Arithmetic-Logic Unit
 - Perform the real work for most instructions here
 - Arithmetic (e.g. **add**, **sub**), Shifting (e.g. **sll**), Logical (e.g. **and**, **or**)
 - Memory operation (e.g. **lw**, **sw**): Address calculation
 - Branch operation (e.g. **bne**, **beq**): Perform register comparison and target address calculation
- Input from previous stage (**Decode**):
 - Operation and Operand(s)
- Output to the next stage (**Memory**):
 - Calculation result

ALU Stage: Block Diagram

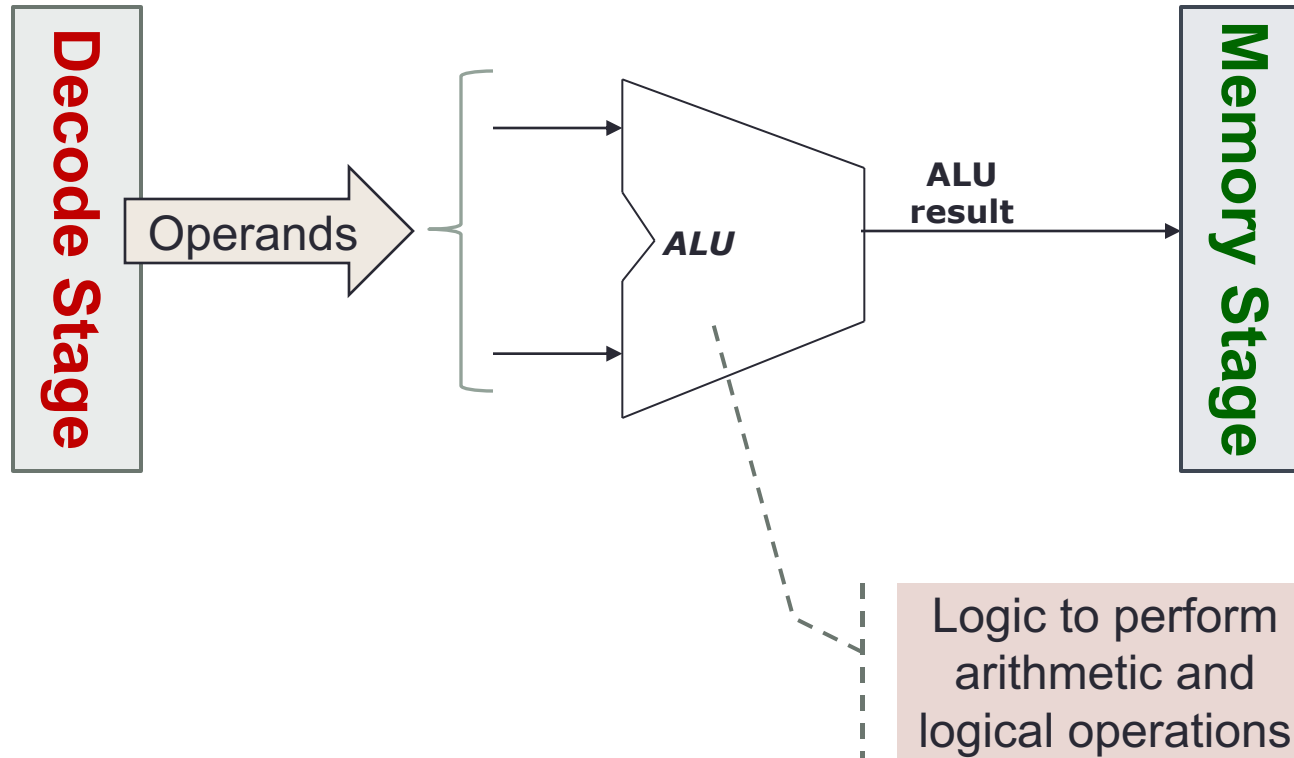

Element: Arithmetic Logical Unit

- **ALU (Arithmetic-logical unit)**

- Combinational logic to implement arithmetic and logical operations

- **Inputs:**


- Two 32-bit numbers

- **Control:**

- 4-bit to decide the particular operation

- **Outputs:**

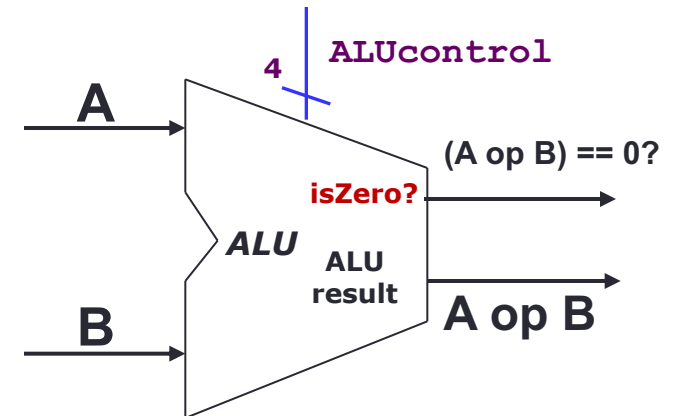- Result of arithmetic/logical operation
- A 1-bit signal to indicate whether result is zero




ALUcontrol	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	slt
1100	NOR

ALU Stage: Non-Branch Instructions

- We can handle non-branch instructions easily:

add \$8, \$9, \$10

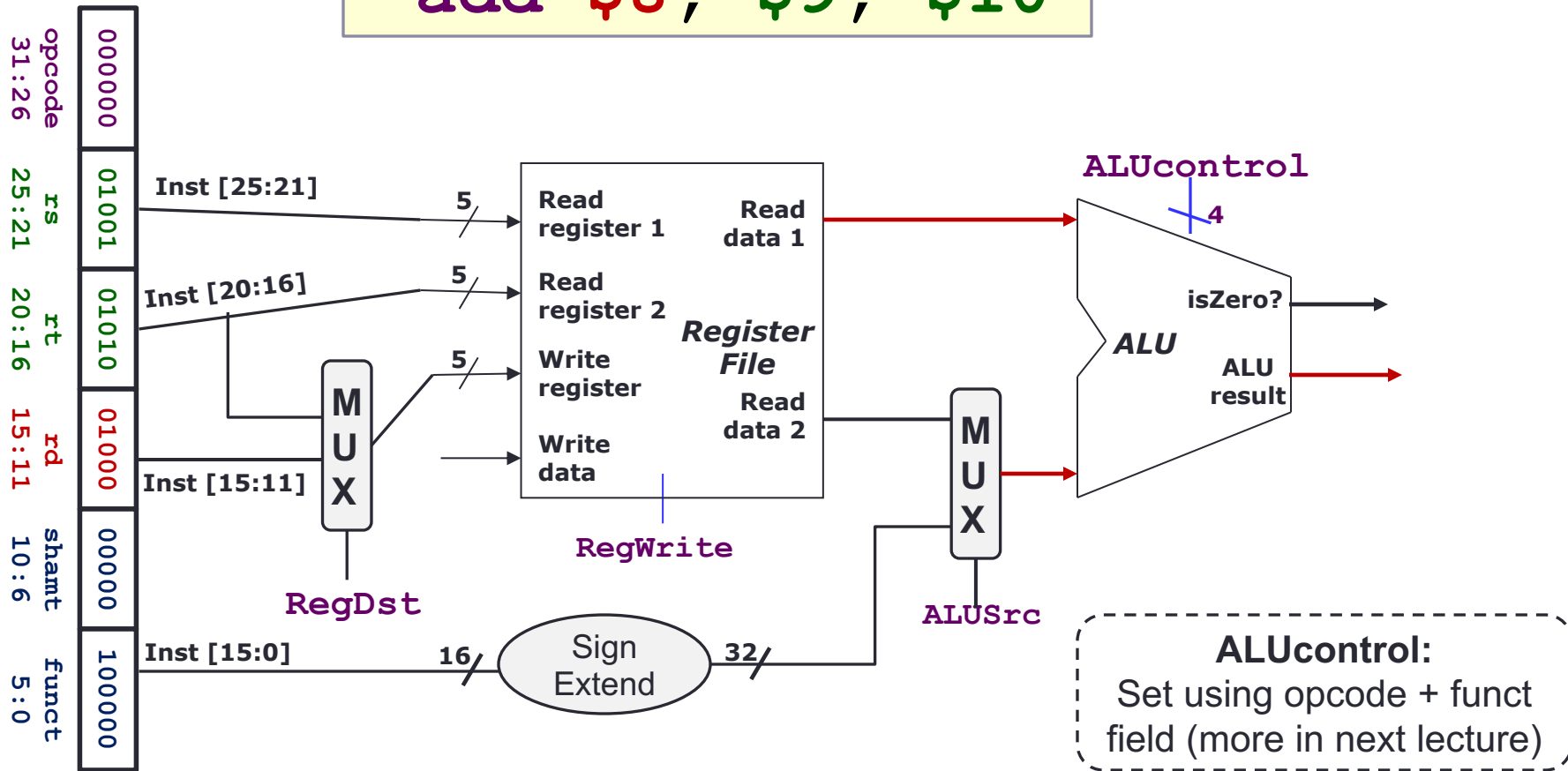

ALU Stage: Branch Instructions

- Branch instruction is harder as we need to perform two calculations:
- Example: "**beq** \$9, \$0, 3"
 1. **Branch Outcome:**
 - Use ALU unit to compare the register
 - The 1-bit "**isZero?**" signal is enough to handle equal / not equal check (how?)
 2. **Branch Target Address:**
 - Introduce additional logic to calculate the address
 - Need **PC** (from Fetch Stage)
 - Need **Offset** (from Decode Stage)

Complete ALU Stage


Fetch

Decode

ALU

Memory

WriteBk

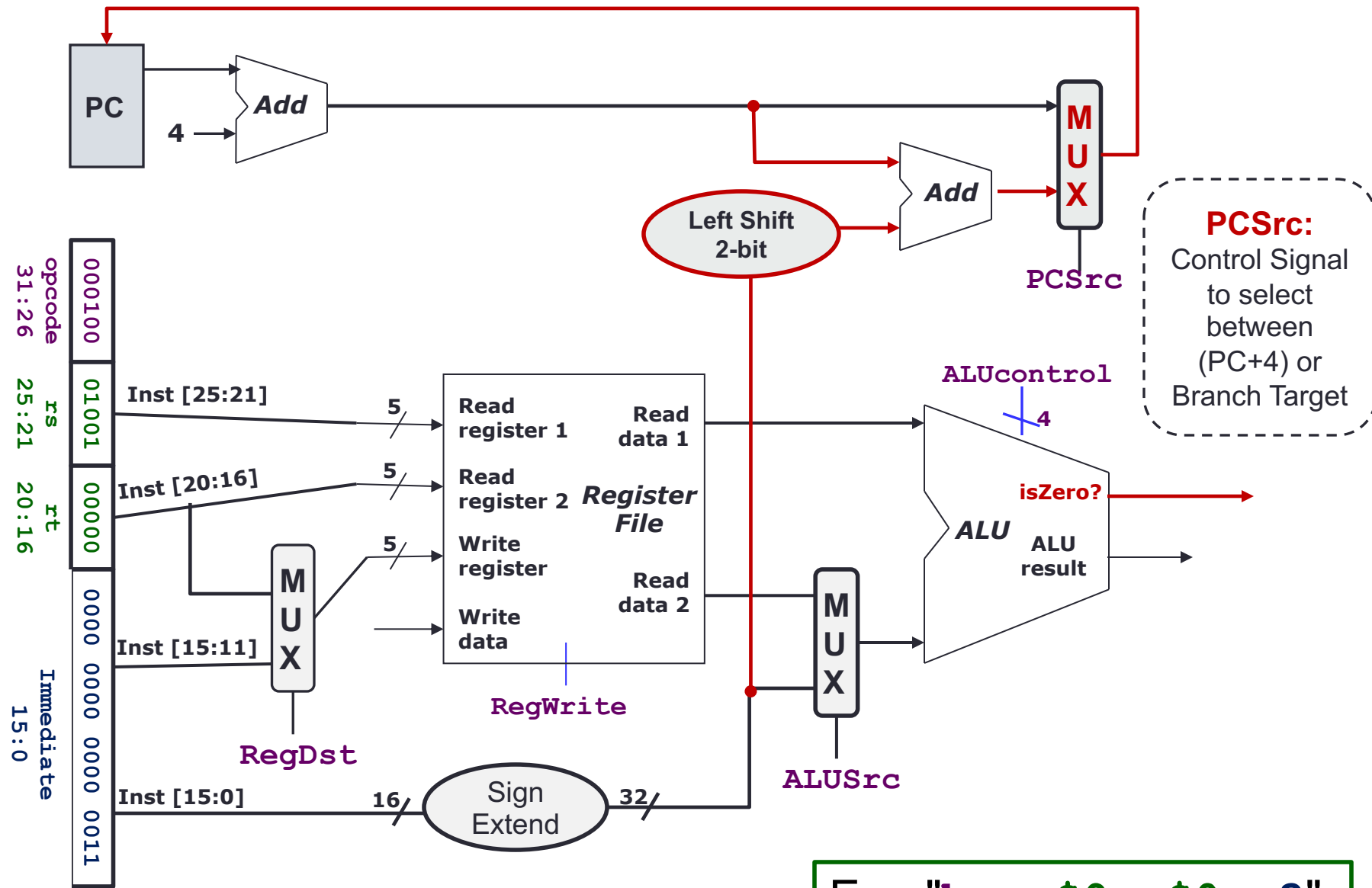


E.g. "beq \$9, \$0, 3"

Memory Stage: Requirement


- Instruction **Memory Access Stage**:
 - Only the load and store instructions need to perform operation in this stage:
 - Use memory address calculated by ALU Stage
 - Read from or write to data memory
 - All other instructions remain idle
 - Result from ALU Stage will pass through to be used in Result Store (Writeback) stage if applicable
- Input from previous stage (**ALU**):
 - Computation result to be used as memory address (if applicable)
- Output to the next stage (**Writeback**):
 - Result to be stored (if applicable)

Memory Stage: Block Diagram

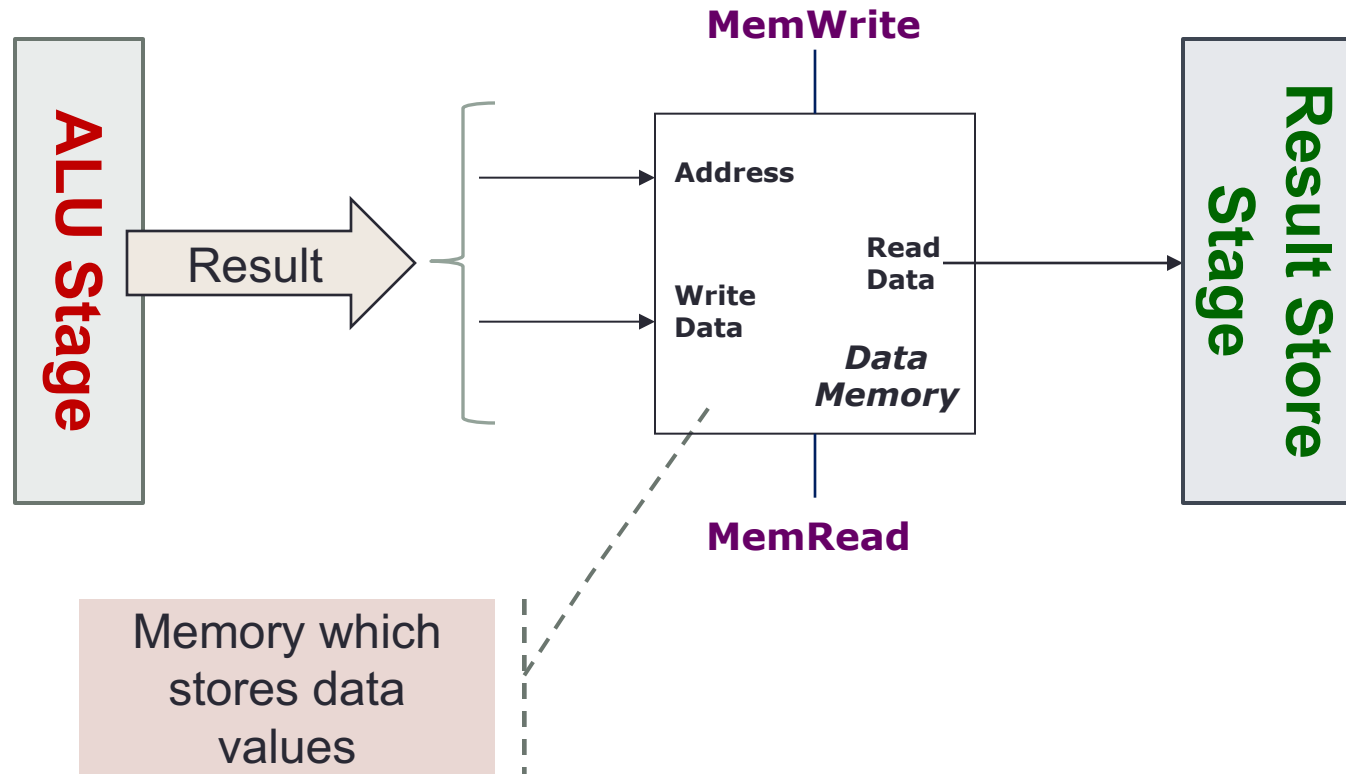

Element: Data Memory

 
- Storage element for the data of a program
- **Inputs:**
 - Memory Address
 - Data to be written (Write Data) for store instructions
- **Control:**
 - Read and Write controls; only one can be asserted at any point of time
- **Output:**
 - Data read from memory (Read Data) for load instructions



Memory Stage: Load Instructions

- Only relevant parts of Decode & ALU Stages are shown


lw \$21, -50(\$22)

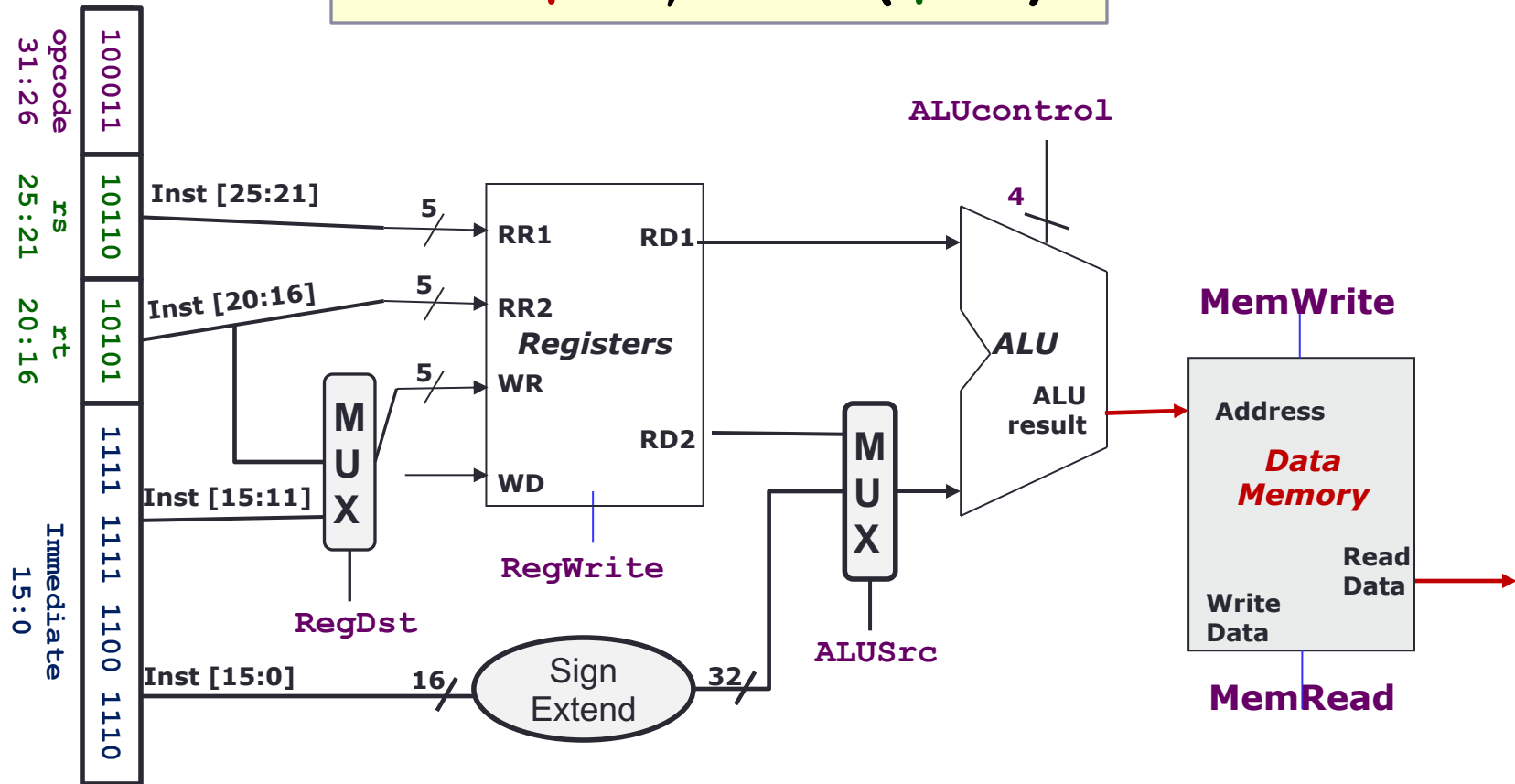

Memory Stage: Store Instructions

- Need *Read Data 2* (Decode) as the *Write Data*


sw \$21, -50 (\$22)

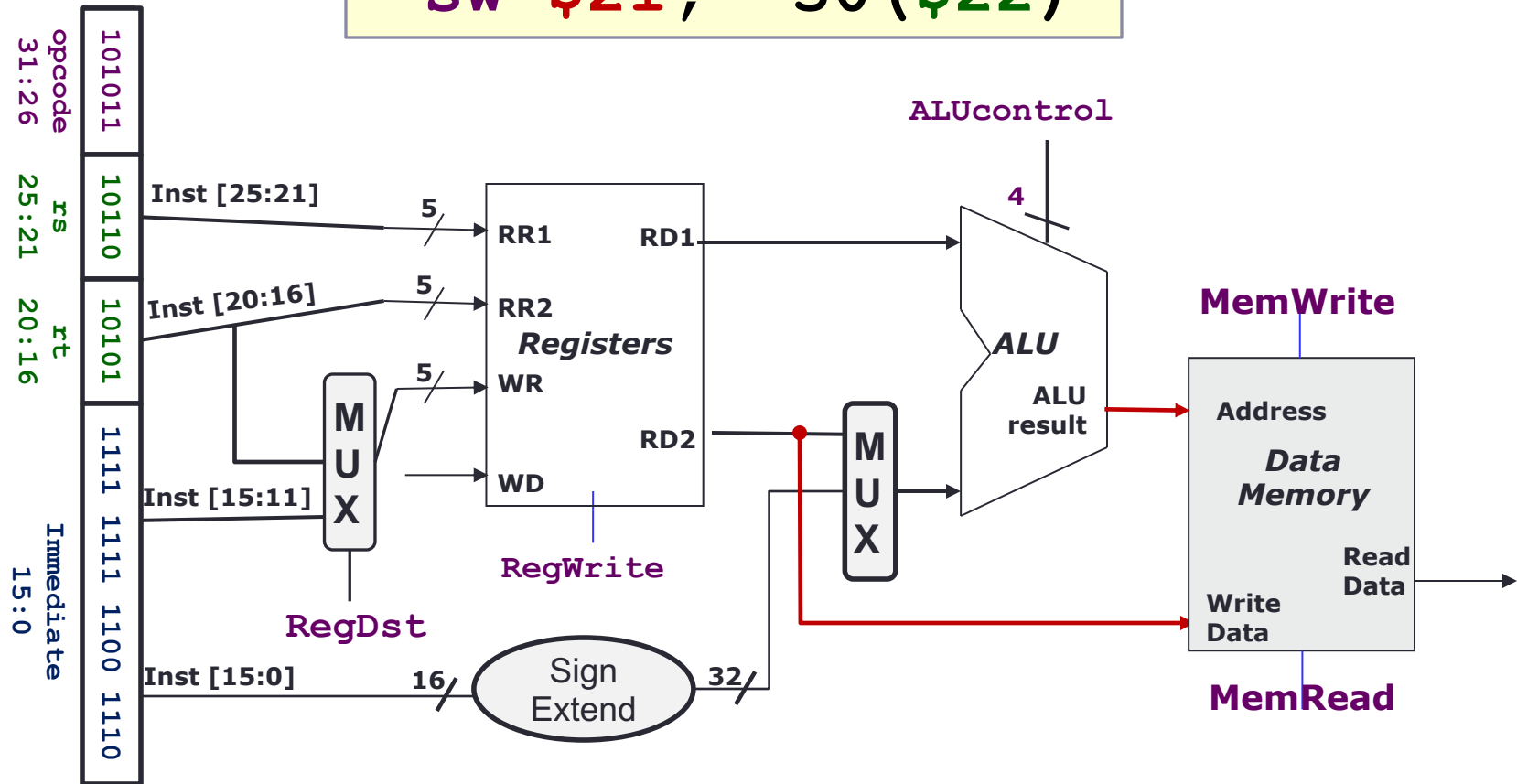

Memory Stage: Non-Memory Instructions

- Add a multiplexer to choose the result to be stored


add \$8, \$9, \$10

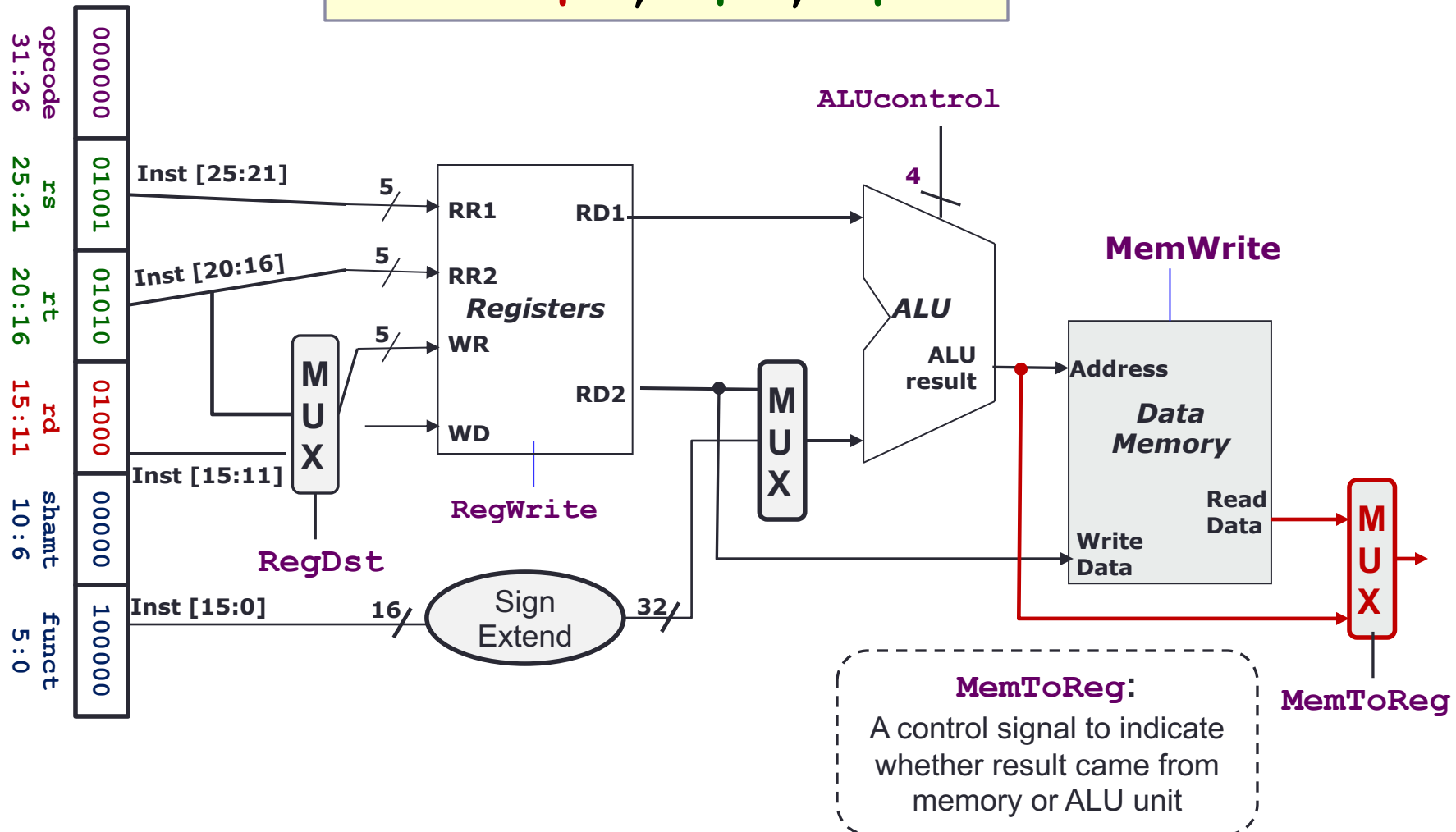

Result Write Stage: Requirement

- Instruction **Register Write Stage**:
 - Most instructions write the result of some computation into a register
 - Examples: arithmetic, logical, shifts, loads, set-less-than
 - Need destination register number and computation result
 - Exceptions are stores, branches, jumps:
 - There are no results to be written
 - These instructions remain idle in this stage
- Input from previous stage (**Memory**):
 - Computation result either from memory or ALU


Result Write Stage: Block Diagram

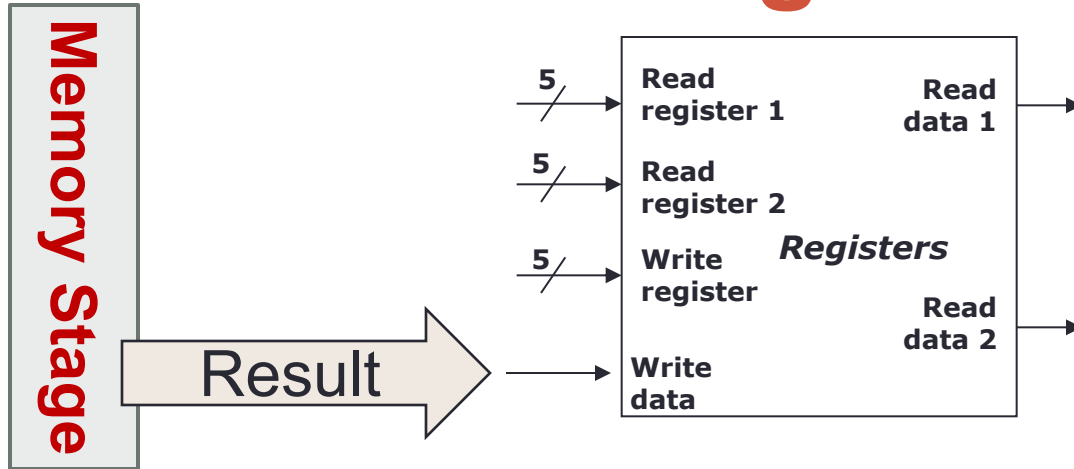

- Result Write stage has no additional element:
 - Basically just route the correct result into register file
 - The **Write Register** number is generated way back in the **Decode Stage**


Result Write Stage: Routing

add \$8, \$9, \$10

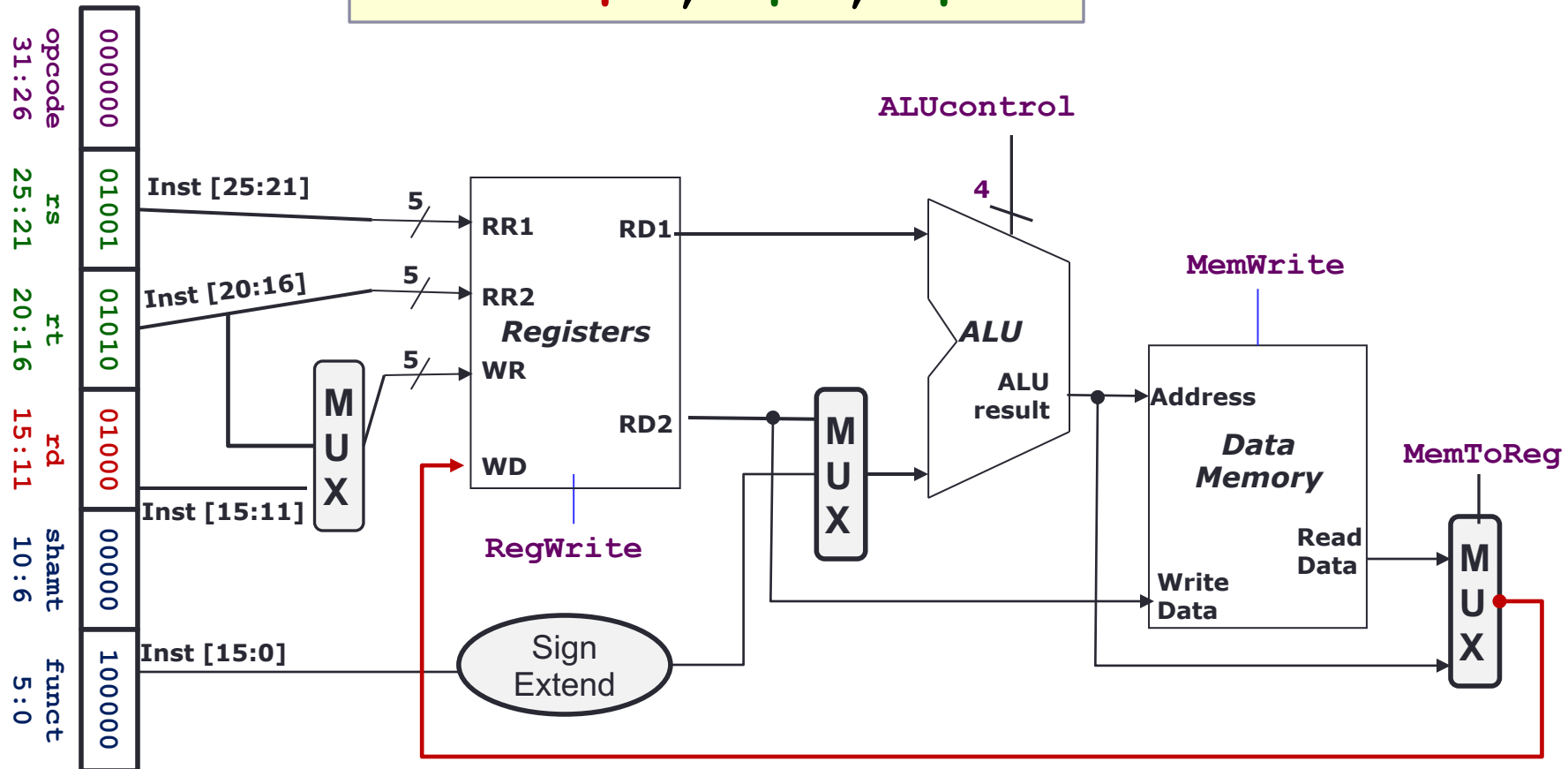


The Complete Datapath!

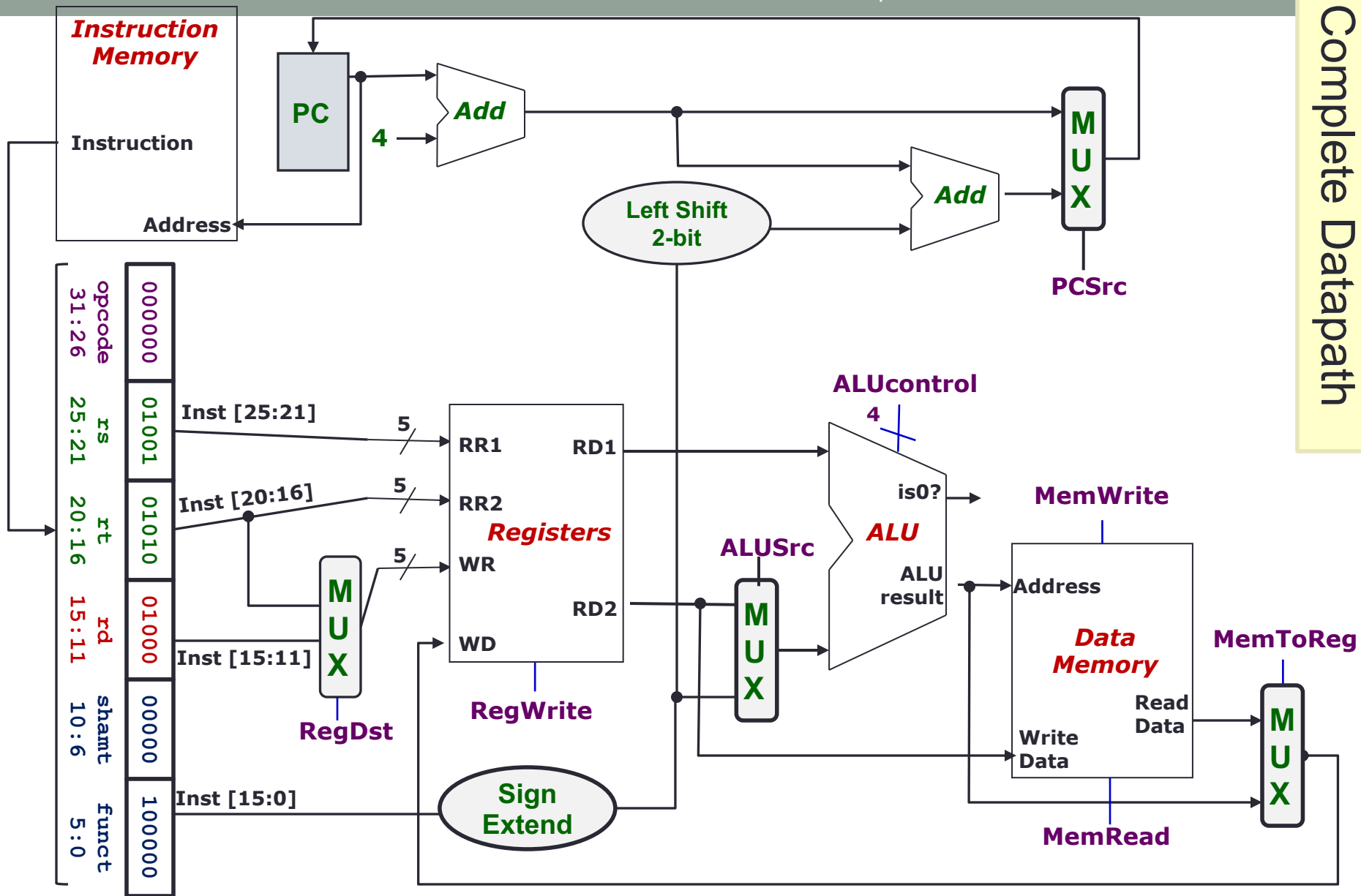- We have just finished “designing” the datapath for a subset of MIPS instructions:
 - Shifting and Jumping are not supported
- Check your understanding:
 - Take the complete datapath and play the role of controller:
 - See how supported instructions are executed
 - Figure out the correct control signals for the datapath elements
- Coming up next: **Control** (Lecture #16)



Datapath: Generic Steps

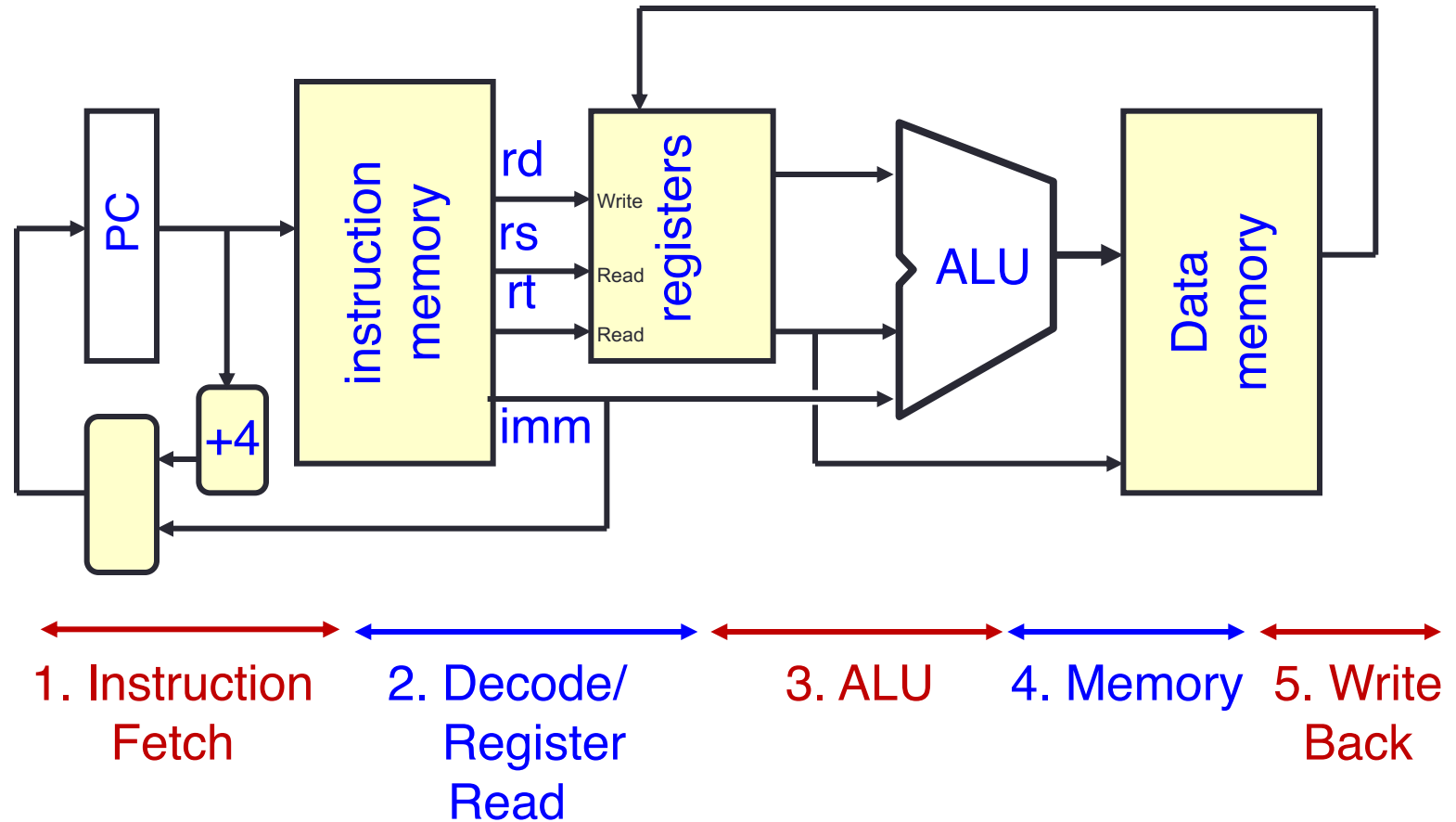


Datapath Walkthroughs: ADD (1/2)

- **add \$r3,\$r1,\$r2 # r3 = r1+r2**
 - Stage 1: Fetch this instruction, increment PC.
 - Stage 2: Decode to find that it is an **add** instruction, then read registers **\$r1** and **\$r2**.
 - Stage 3: Add the two values retrieved in stage 2.
 - Stage 4: Idle (nothing to write to memory).
 - Stage 5: Write result of stage 3 into register **\$r3**.

Datapath Walkthroughs: ADD (2/2)

`add $r3, $r1, $r2`

 


Datapath Walkthroughs: SLTI (1/2)

- **slti \$r3,\$r1,17**
 - Stage 1: Fetch this instruction, increment PC.
 - Stage 2: Decode to find it is an **slti**, then read register **\$r1**.
 - Stage 3: Compare value retrieved in stage 2 with the integer 17.
 - Stage 4: Go idle.
 - Stage 5: Write the result of stage 3 in register **\$r3**.

Datapath Walkthroughs: SLTI (2/2)

`slti $r3, $r1, 17`

 


Datapath Walkthroughs: SW (1/2)

- **sw \$r3, 20(\$r1)**
 - Stage 1: Fetch this instruction, increment PC.
 - Stage 2: Decode to find it is an **sw**, then read registers **\$r1** and **\$r3**.
 - Stage 3: Add 20 to value in register **\$r1** (retrieved in stage 2).
 - Stage 4: Write value in register **\$r3** (retrieved in stage 2) into memory address computed in stage 3.
 - Stage 5: Go idle (nothing to write into a register).

Datapath Walkthroughs: SW (2/2)

`sw $r3, 20($r1)`

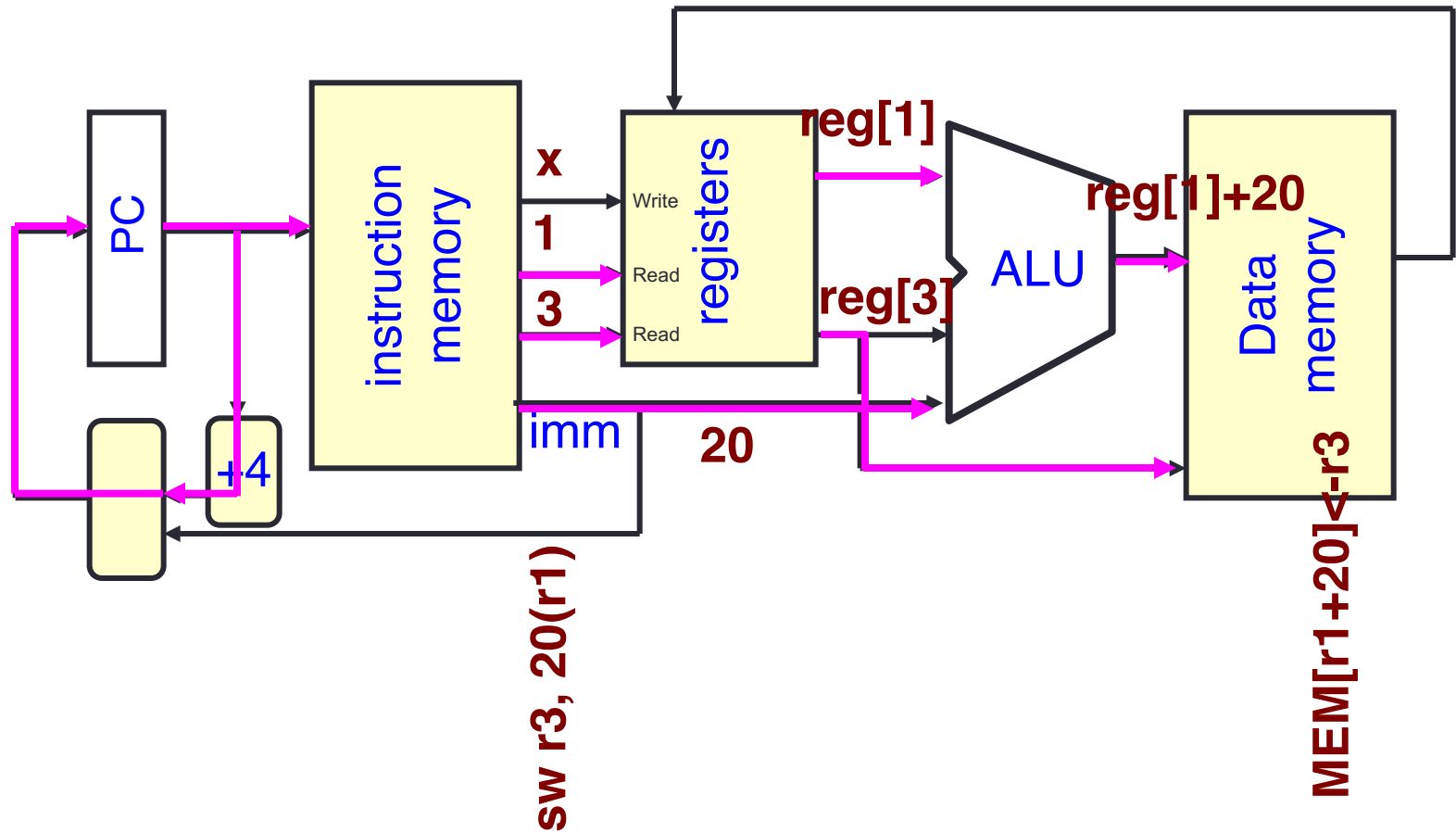

Why Five Stages?


- Could we have a different number of stages?
 - Yes, and other architectures do.
- So why does MIPS have five stages, if instructions tend to go idle for at least one stage?
 - There is one instruction that uses all five stages: the load.

Datapath Walkthroughs: LW (1/2)

- **lw \$r3, 40(\$r1)**
 - Stage 1: Fetch this instruction, increment PC.
 - Stage 2: Decode to find it is a **lw**, then read register **\$r1**.
 - Stage 3: Add 40 to value in register **\$r1** (retrieved in stage 2).
 - Stage 4: Read value from memory address compute in stage 3.
 - Stage 5: Write value found in stage 4 into register **\$r3**.

Datapath Walkthroughs: LW (2/2)

`lw $r3, 40($r1)`

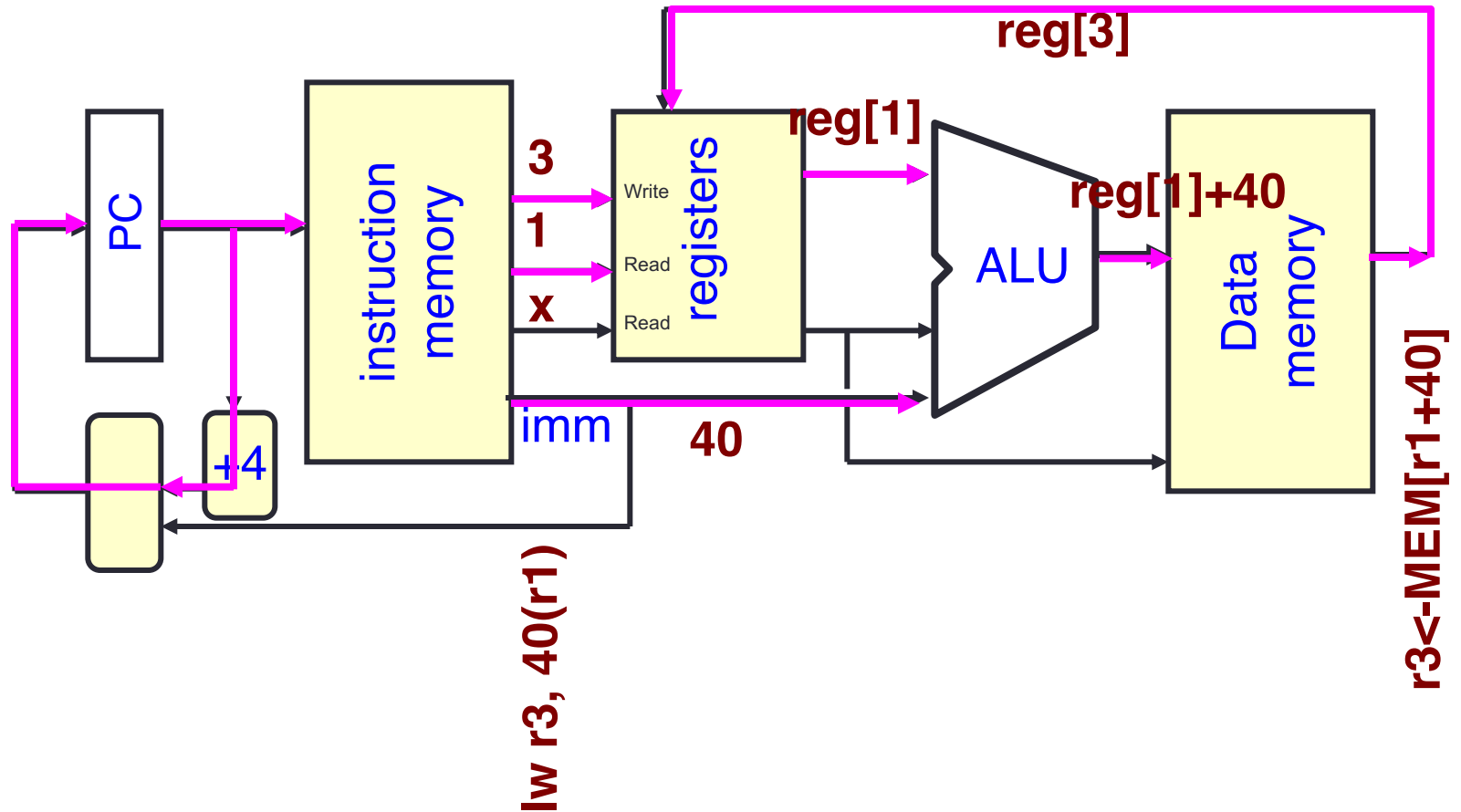


What Hardware is Needed?

- **PC**: a register which keeps track of address of the next instruction.
- **General Purpose Registers**
 - Used in stage 2 (read registers) and stage 5 (writeback).
- **Memory**
 - Used in stage 1 (fetch) and stage 4 (memory).
 - Cache system makes these two stages as fast as the others, on average.

Datapath: Summary

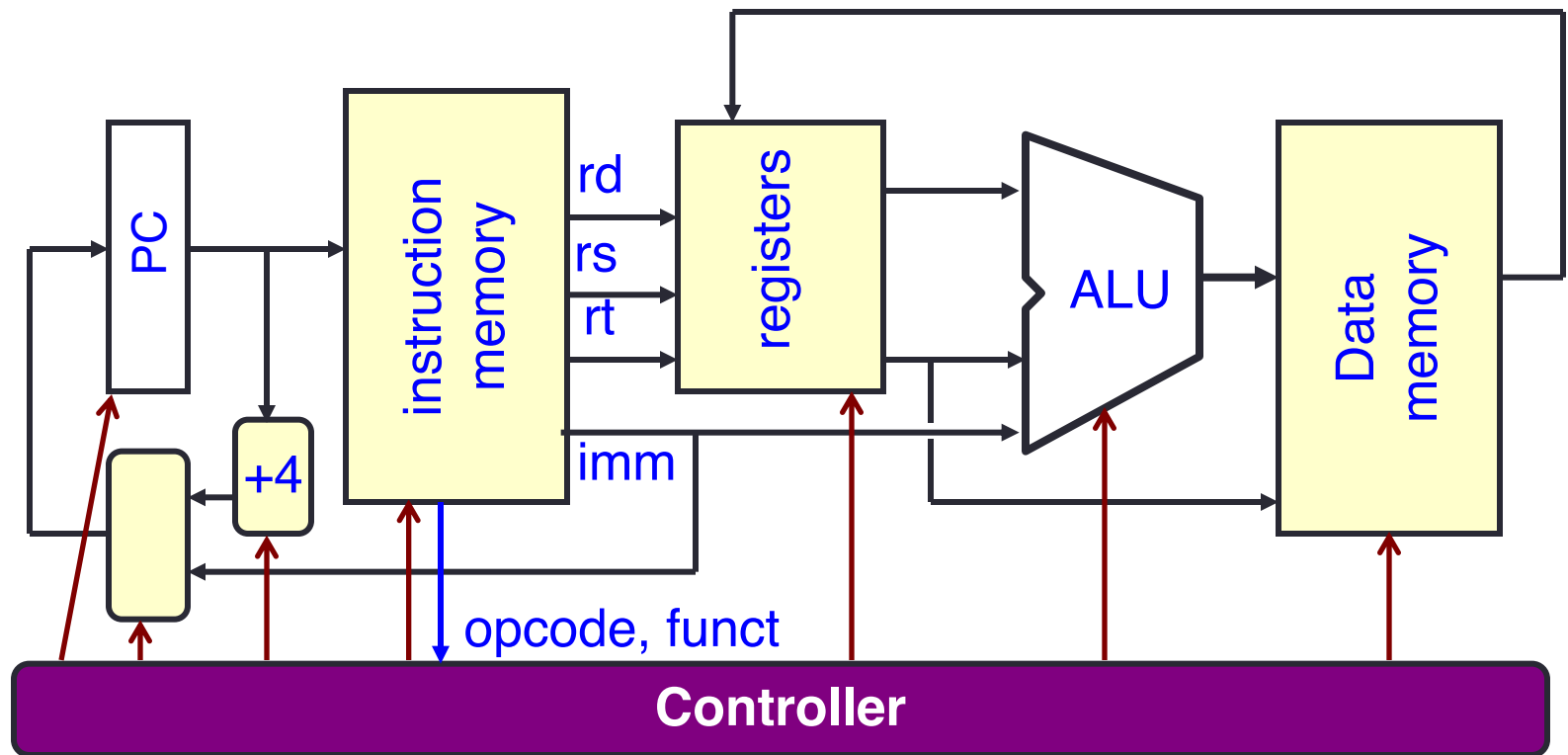- Construct datapath based on register transfers required to perform instructions.
- Control part causes the right transfers to happen.



Reading Assignment

- The Processor: Datapath and Control
 - 3rd edition: Chapter 5 Sections 5.1 – 5.3
 - 4th edition: Chapter 4 Sections 4.1 – 4.3



Q&A