



COMPUTER ORGANISATION (TỔ CHỨC MÁY TÍNH)

Combinational Circuits

Acknowledgement

- The contents of these slides have origin from School of Computing, National University of Singapore.
- We greatly appreciate support from Mr. Aaron Tan Tuck Choy for kindly sharing these materials.

Policies for students

- These contents are only used for students PERSONALLY.
- Students are NOT allowed to modify or deliver these contents to anywhere or anyone for any purpose.

WHERE ARE WE NOW?


- Number systems and codes
 - Boolean algebra
 - Logic gates and circuits
 - Simplification
 - **Combinational circuits**
 - Sequential circuits
 - Performance
 - Assembly language
 - The processor: Datapath and control
 - Pipelining
 - Memory hierarchy: Cache
 - Input/output
-
- Preparation: 2 weeks
- Logic Design: 3 weeks
- Computer organisation

COMBINATIONAL CIRCUITS

- Introduction
- Analysis Procedure
- Design Methods
- Gate-level (SSI) Design
- Block-Level Design
- Arithmetic Circuits
- Circuit Delays
- Look-Ahead Carry Adder


INTRODUCTION

 - Two classes of logic circuits
 - Combinational
 - Sequential
- **Combinational Circuit**
 - Each output depends entirely on the immediate (present) inputs.




■ Sequential Circuit

 - Each output depends on both present inputs and state.



ANALYSIS PROCEDURE

 - Given a combinational circuit, how do you analyze its function?



Steps:

1. Label the inputs and outputs.
2. Obtain the functions of intermediate points and the outputs.
3. Draw the truth table.
4. Deduce the functionality of the circuit ➡


A	B	(A+B)	(A'+B')	F1	F2
0	0	0	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1

DESIGN METHODS

- Different combinational circuit design methods:
 - Gate-level design method (with logic gates)
 - Block-level design method (with functional blocks)
- Design methods make use of logic gates and useful function blocks
 - These are available as Integrated Circuit (IC) chips.
 - Types of IC chips (based on packing density): SSI, MSI, LSI, VLSI, ULSI.
- Main objectives of circuit design:
 - Reduce cost (number of gates for small circuits; number of IC packages for complex circuits)
 - Increase speed
 - Design simplicity (re-use blocks where possible)

GATE-LEVEL (SSI) DESIGN: HALF ADDER (1/2)

 - Design procedure:
 - State problem
Example: Build a **Half Adder**.
 - Determine and label the inputs and outputs of circuit.
Example: Two inputs and two outputs labelled, as shown below.



X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Draw the truth table.

GATE-LEVEL (SSI) DESIGN: HALF ADDER (2/2)


4. Obtain simplified Boolean functions.

Example: $C = X \cdot Y$

$$S = X' \cdot Y + X \cdot Y' = X \oplus Y$$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

5. Draw logic diagram.

 

Half Adder


GATE-LEVEL (SSI) DESIGN: FULL ADDER (1/5)

- Half adder adds up only two bits.
- To add two binary numbers, we need to add 3 bits (including the *carry*).

- Example:

	1	1	1		carry
	0	0	1	1	X
+	0	1	1	1	Y
	1	0	1	0	S

 - Need **Full Adder** (so called as it can be made from two half adders).



GATE-LEVEL (SSI) DESIGN: FULL ADDER (2/5)

- Truth table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z - carry in (to the current position)

C - carry out (to the next position)

- Using K-map, simplified SOP form:

C = ?

S = ?

C

YZ	00	01	11	10
X				
0			1	
1		1	1	1

S

YZ	00	01	11	10
X				
0		1		1
1	1		1	

GATE-LEVEL (SSI) DESIGN: FULL ADDER (3/5)

- Alternative formulae using algebraic manipulation:

$$\begin{aligned}C &= X \cdot Y + X \cdot Z + Y \cdot Z \\&= X \cdot Y + (X + Y) \cdot Z \\&= X \cdot Y + ((X \oplus Y) + X \cdot Y) \cdot Z \\&= X \cdot Y + (X \oplus Y) \cdot Z + X \cdot Y \cdot Z \\&= \mathbf{X \cdot Y + (X \oplus Y) \cdot Z}\end{aligned}$$


$$\begin{aligned}S &= X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z \\&= X' \cdot (Y' \cdot Z + Y \cdot Z') + X \cdot (Y' \cdot Z' + Y \cdot Z) \\&= X' \cdot (Y \oplus Z) + X \cdot (Y \oplus Z)' \\&= \mathbf{X \oplus (Y \oplus Z)}\end{aligned}$$

GATE-LEVEL (SSI) DESIGN: FULL ADDER (4/5)

- Circuit for above formulae:

$$C = X \cdot Y + (X \oplus Y) \cdot Z$$
 
$$S = X \oplus (Y \oplus Z) = (X \oplus Y) \oplus Z \text{ (XOR is associative)}$$




Full Adder made from two Half-Adders (+ an OR gate).

GATE-LEVEL (SSI) DESIGN: FULL ADDER (5/5)

- Circuit for above formulae:

$$C = X \cdot Y + (X \oplus Y) \cdot Z$$


$$S = X \oplus (Y \oplus Z)$$

 

Full Adder made from two Half-Adders (+ an OR gate).

CODE CONVERTERS

 - **Code converter** – takes an input code, translates to its equivalent output code.







- Example: **BCD to Excess-3 code converter.**
 - Input: BCD code
 - Output: Excess-3 code

BCD-TO-EXCESS-3 CONVERTER (1/2)

• Truth table:

	<i>BCD</i>				<i>Excess-3</i>			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

■ K-maps:

    

BCD-TO-EXCESS-3 CONVERTER (2/2)

		C			
		CD		01	11
A	AB	00	01	11	10
	00				
	01		1	1	1
	11	X	X	X	X
	10	1	1	X	X

W **D**

		C			
		CD		01	11
A	AB	00	01	11	10
	00		1	1	1
	01	1			
	11	X	X	X	X
	10		1	X	X

X **D**

W = ?

X = ?

Y = ?

Z = ?

		C			
		CD		01	11
A	AB	00	01	11	10
	00	1		1	
	01	1		1	
	11	X	X	X	X
	10	1		X	X

Y **D**

		C			
		CD		01	11
A	AB	00	01	11	10
	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X


Z **D**

BLOCK-LEVEL DESIGN

- More complex circuits can also be built using **block-level** method.
- In general, block-level design method (as opposed to gate-level design) relies on algorithms or formulae of the circuit, which are obtained by decomposing the main problem to sub-problems recursively (until small enough to be directly solved by blocks of circuits).
- Simple examples using 4-bit parallel adder as building blocks:
 1. **BCD-to-Excess-3 Code Converter**
 2. **16-bit Parallel Adder**
 3. **Adder cum Subtractor**

4-BIT PARALLEL ADDER (1/4)

 - Consider a circuit to add two 4-bit numbers together and a carry-in, to produce a 5-bit result.



- 5-bit result is sufficient because the largest result is:
 $1111_2 + 1111_2 + 1_2 = 11111_2$

4-BIT PARALLEL ADDER (2/4)

- SSI design technique should not be used here.
- Truth table for 9 inputs is too big: $2^9 = 512$ rows!

$X_4X_3X_2X_1$	$Y_4Y_3Y_2Y_1$	C_1	C_5	$S_4S_3S_2S_1$
0 0 0 0	0 0 0 0	0	0	0 0 0 0
0 0 0 0	0 0 0 0	1	0	0 0 0 1
0 0 0 0	0 0 0 1	0	0	0 0 0 1
...
0 1 0 1	1 1 0 1	1	1	0 0 1 1
...
1 1 1 1	1 1 1 1	1	1	1 1 1 1

- Simplification becomes too complicated!

4-BIT PARALLEL ADDER (3/4)

- Alternative design possible.
- Addition formula for each pair of bits (with carry in),

$$C_{i+1}S_i = X_i + Y_i + C_i$$

has the same function as a full adder:


$$C_{i+1} = X_i \cdot Y_i + (X_i \oplus Y_i) \cdot C_i$$

$$S_i = X_i \oplus Y_i \oplus C_i$$

$$\begin{array}{rcl} C = & & 1\ 1\ 0\ 0 \\ X = & & 1\ 0\ 1\ 0 \\ Y = & & 1\ 1\ 1\ 1 \\ X + Y = & 1\ 1\ 0\ 0\ 1 \end{array}$$

4-BIT PARALLEL ADDER (4/4)

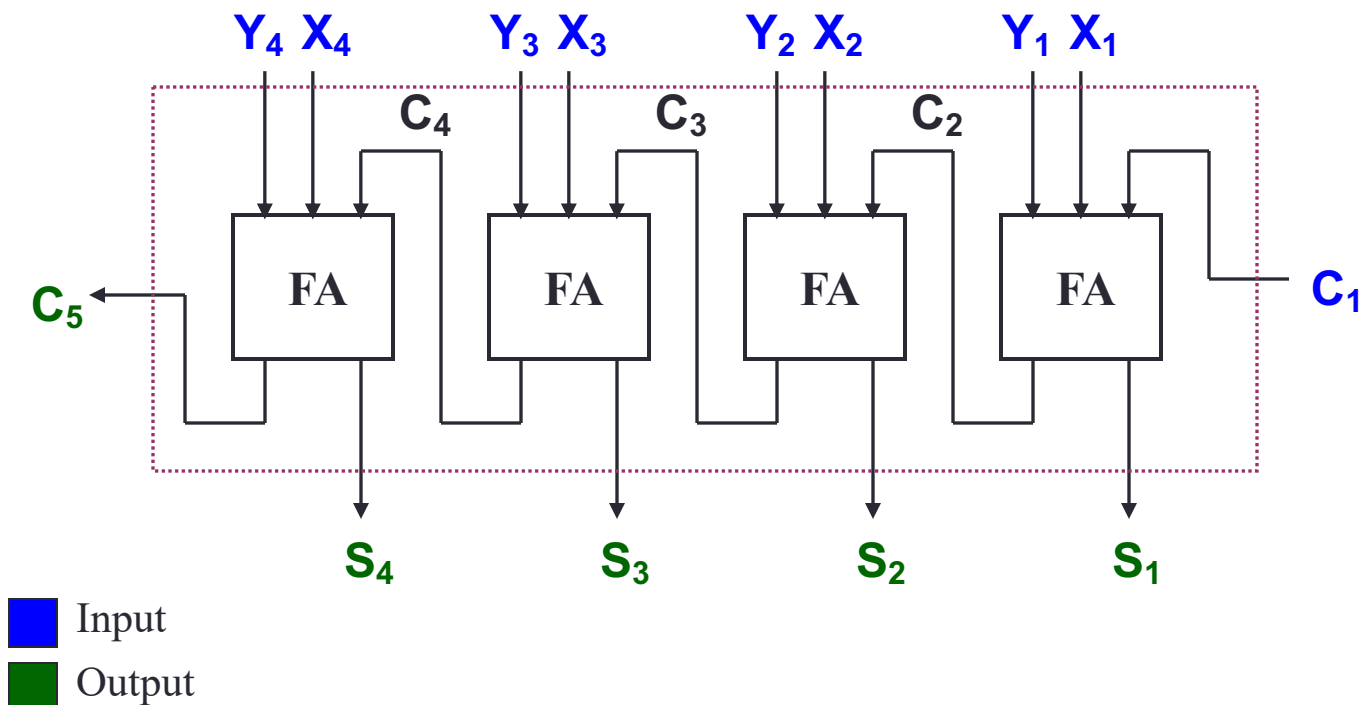- Cascading 4 full adders via their carries, we get:



PARALLEL ADDERS

- Note that carry is propagated by cascading the carry from one full adder to the next.
- Called **Parallel Adder** because inputs are presented simultaneously (in parallel). Also called **Ripple-Carry Adder**.

BCD-TO-EXCESS-3 CONVERTER (1/2)


- Excess-3 code can be converted from BCD code using truth table:
- Gate-level design can be used since only 4 inputs.
- However, alternative design is possible.
- Use problem-specific formula:

$$\begin{aligned} \text{Excess-3 code} \\ = \text{BCD Code} + 0011_2 \end{aligned}$$

	<i>BCD</i>				<i>Excess-3</i>			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X


BCD-TO-EXCESS-3 CONVERTER (2/2)

- Block-level circuit:

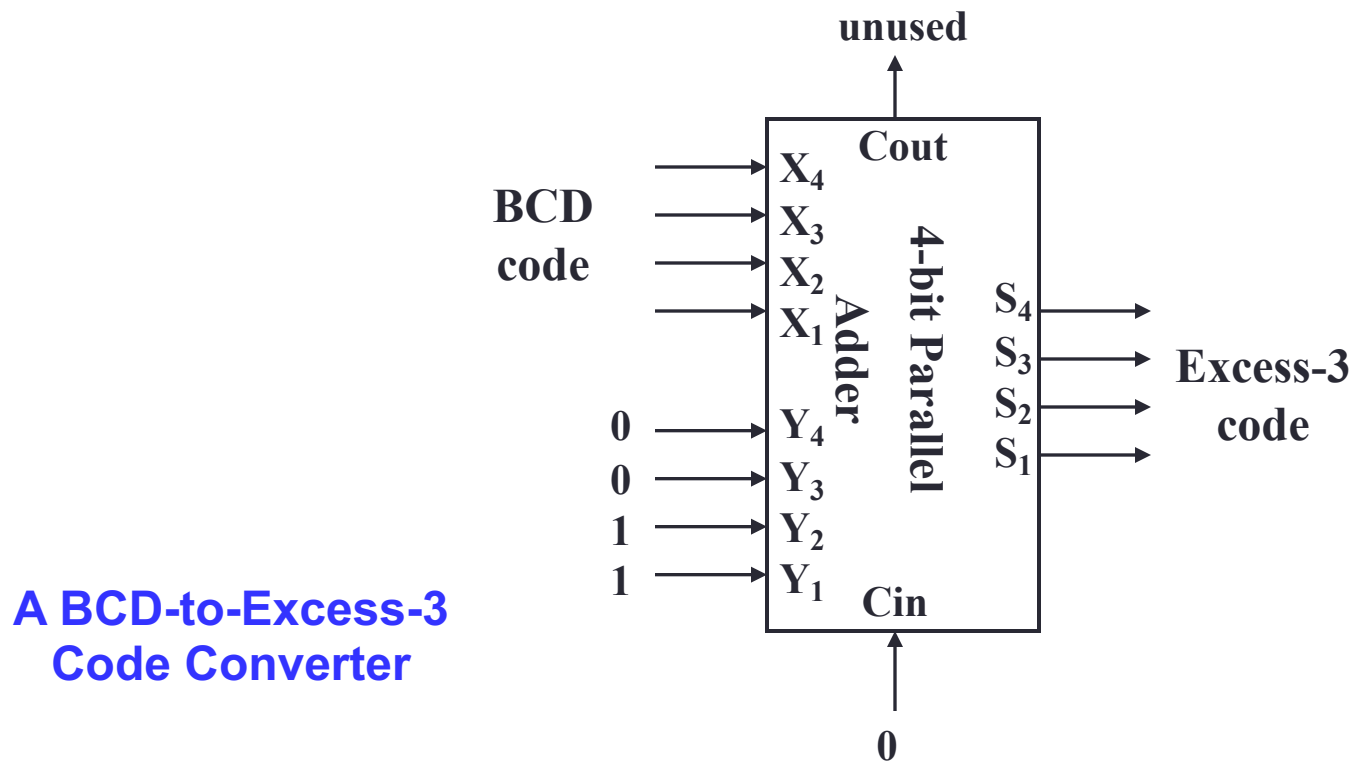


16-BIT PARALLEL ADDER

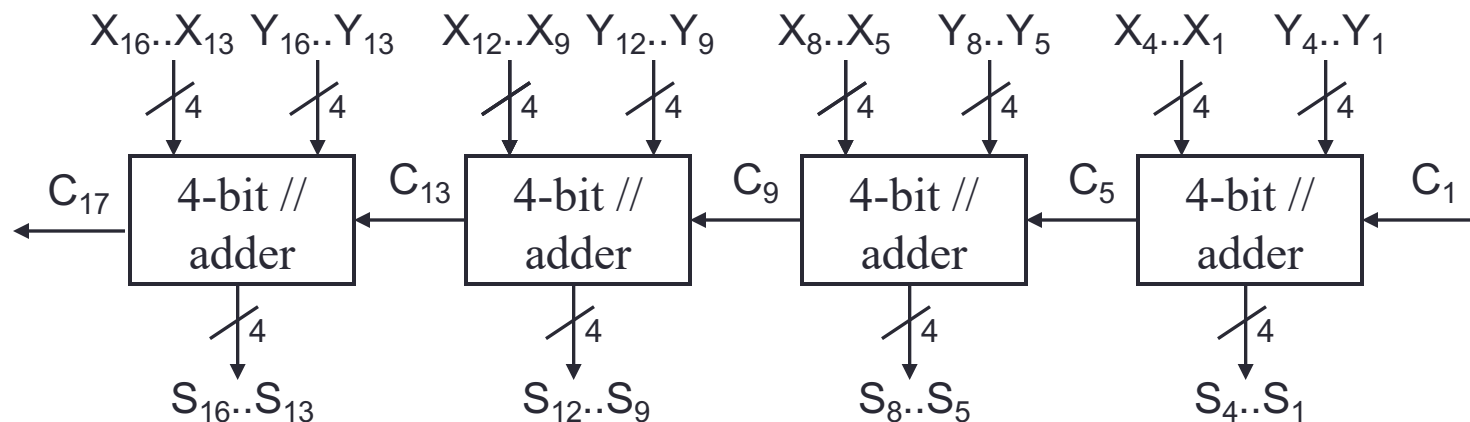- Larger parallel adders can be built from smaller ones.
- Example: A **16-bit parallel adder** can be constructed from four 4-bit parallel adders:




A 16-bit parallel adder

 

4-BIT ADDER CUM SUBTRACTOR (1/3)

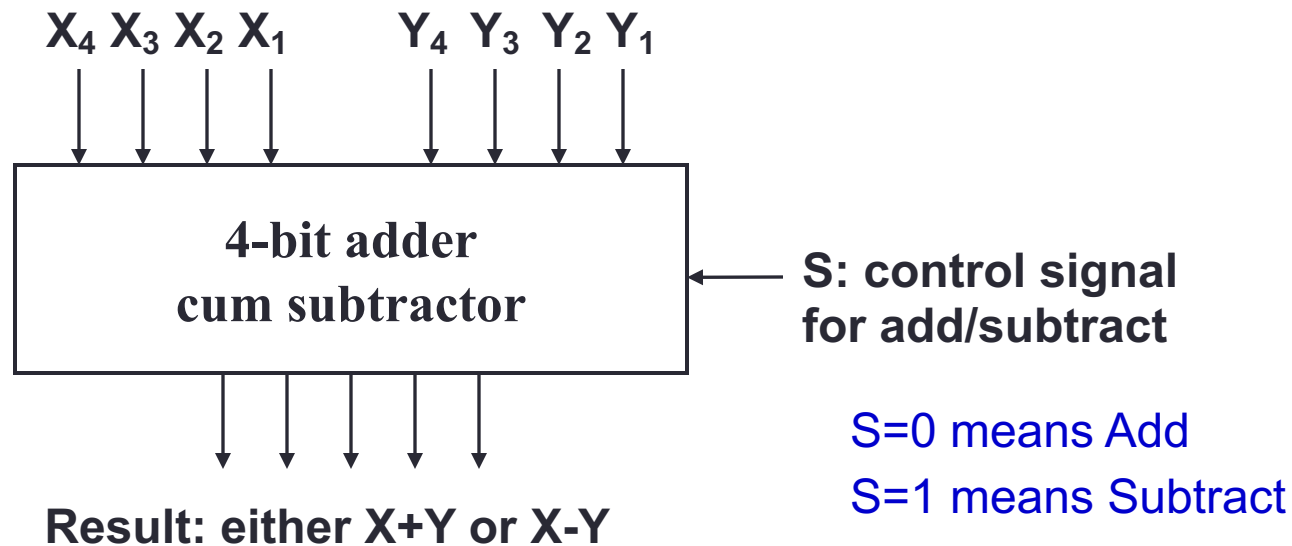- Recall: Subtraction can be done via addition with 2s-complement numbers.
- Hence, we can design a circuit to perform **both addition and subtraction**, using a parallel adder and some gates.



4-BIT ADDER CUM SUBTRACTOR (2/3)

- Recall:


$$\begin{aligned}X - Y &= X + (-Y) \\&= X + (2\text{s complement of } Y) \\&= X + (1\text{s complement of } Y) + 1\end{aligned}$$

- Design requires:

(1) **XOR gates**, and (2) **S connected to carry-in**.

4-BIT ADDER CUM SUBTRACTOR (3/3)






- 4-bit adder-cum-subtractor circuit:

 

REVISION: HALF ADDER

- Half adder



x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

     

REVISION: FULL ADDER

- Full adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  


yz \ x	00	01	11	10
0			1	
1		1	1	1

$$C = xy + xz + yz$$

yz \ x	00	01	11	10
0		1		1
1	1		1	

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 



REVISION: PARALLEL ADDER

- 4-bit parallel adder

Subscript i	4	3	2	1	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}


2 ways:

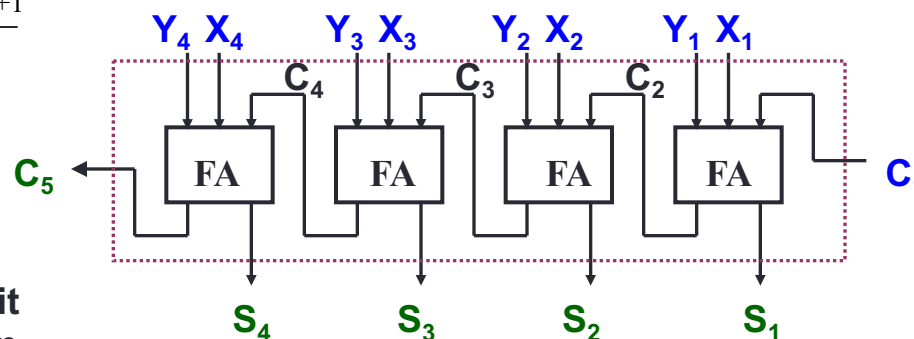 - Serial (one FA)
- Parallel (n FAs for n bits)




REVISION: CASCADING ADDERS

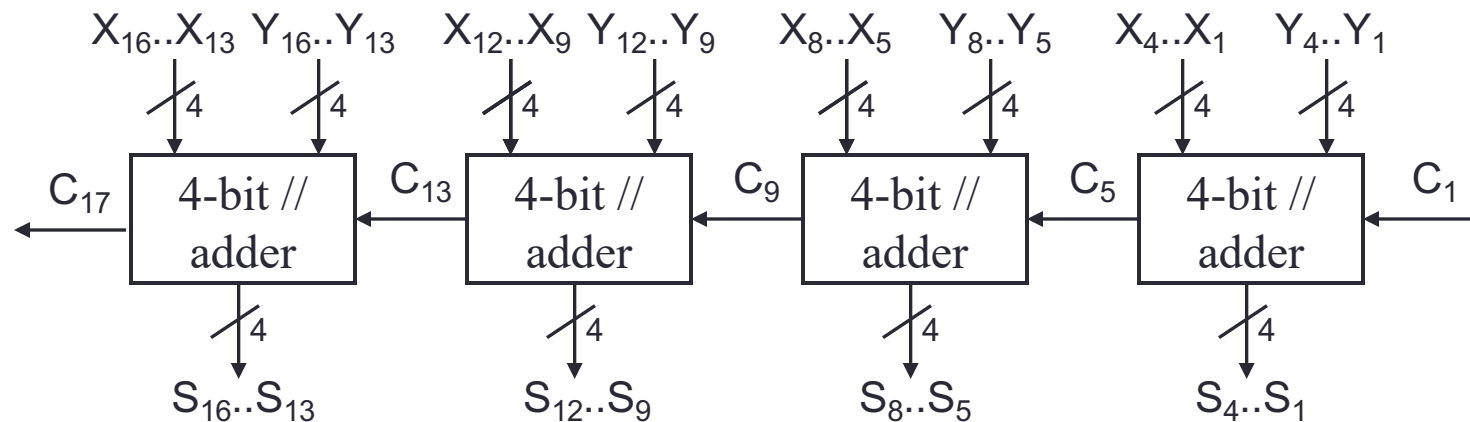- Cascading 4 full adders (FAs) gives a 4-bit parallel adder.
 - Classical method: 9 input variables $\rightarrow 2^9 = 512$ rows in truth table!
- Cascading method can be extended to larger adders.
 - Example: **16-bit parallel adder**.



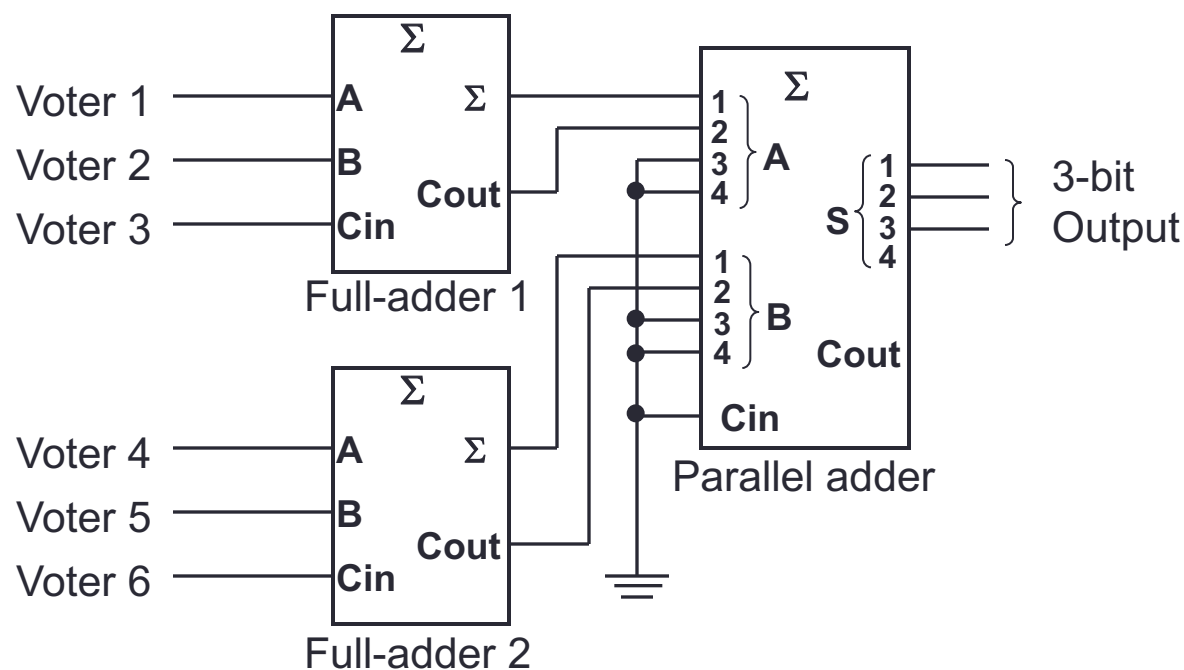EXAMPLE

- Application: **6-person voting system.**
 - Use FAs and a 4-bit parallel adder.
 - Each FA can sum up to 3 votes.




MAGNITUDE COMPARATOR (1/4)

- **Magnitude comparator**: compares 2 values A and B , to check if $A > B$, $A = B$, or $A < B$.
- To design an n -bit magnitude comparator using classical method, it would require 2^{2n} rows in truth table!
- We shall exploit regularity in our design.
- Question: How do we compare two 4-bit values A ($a_3a_2a_1a_0$) and B ($b_3b_2b_1b_0$)?


MAGNITUDE COMPARATOR (2/4)

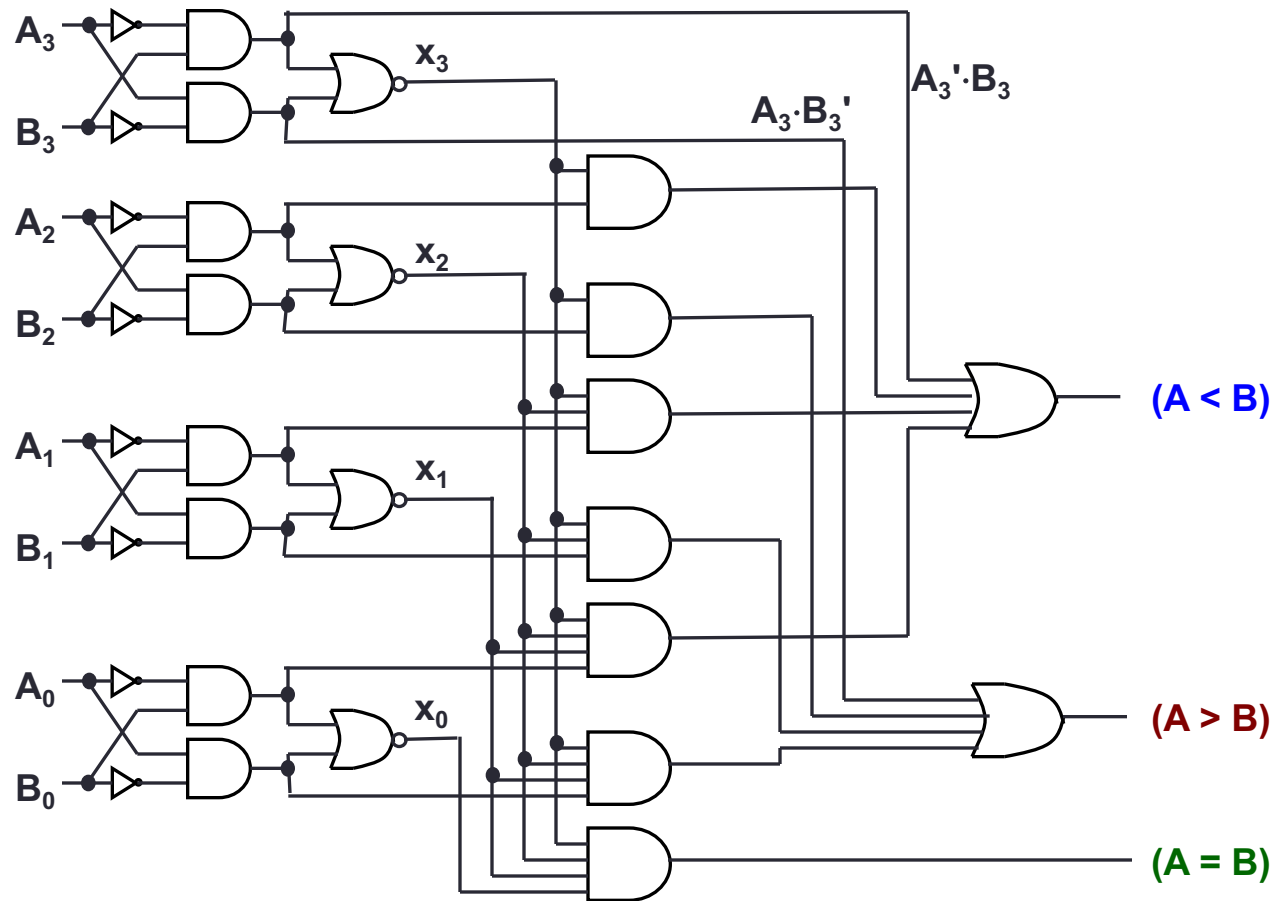Let $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$; $x_i = A_i \cdot B_i + A_i' \cdot B_i'$





MAGNITUDE COMPARATOR (3/4)

 - Block diagram of a 4-bit magnitude comparator



MAGNITUDE COMPARATOR (4/4)

  
- A function F accepts a 4-bit binary value $ABCD$, and returns 1 if $3 \leq ABCD \leq 12$, or 0 otherwise. How would you implement F using magnitude comparators and a suitable logic gate?



CIRCUIT DELAYS (1/5)

- Given a logic gate with delay t . If inputs are stable at times t_1, t_2, \dots, t_n , then the earliest time in which the output will be stable is:


$$\max(t_1, t_2, \dots, t_n) + t$$

 

- To calculate the delays of all outputs of a combinational circuit, repeat above rule for all gates.


CIRCUIT DELAYS (2/5)

 - As a simple example, consider the full adder circuit where all inputs are available at time 0. Assume each gate has delay t .



CIRCUIT DELAYS (3/5)

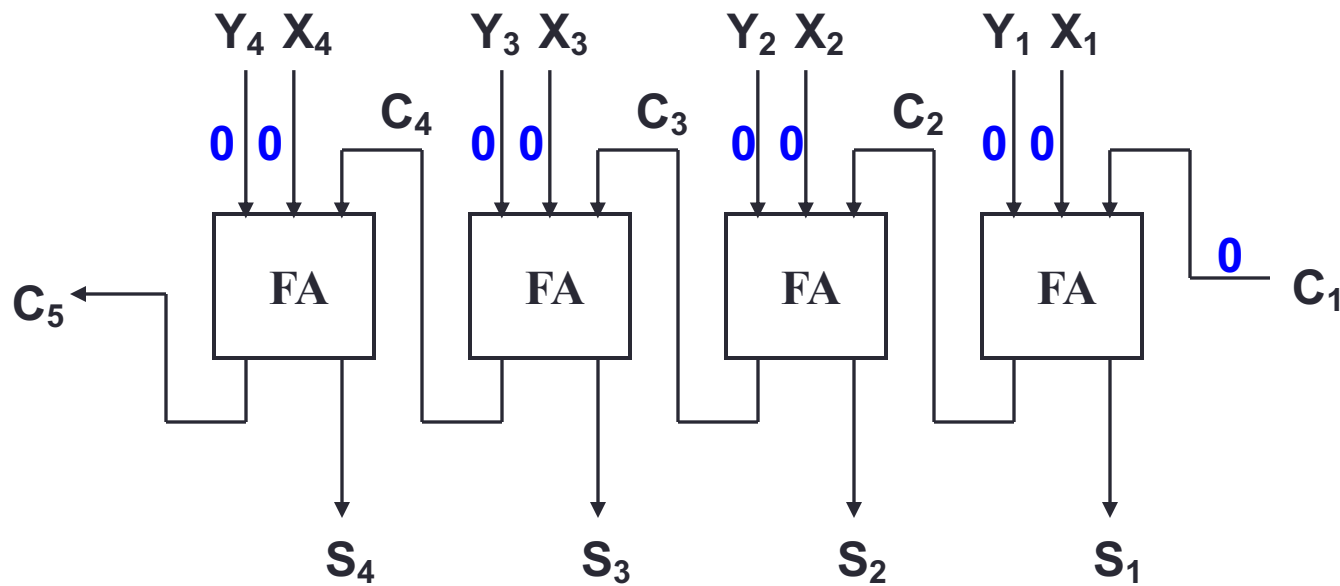- More complex example: 4-bit parallel adder.




CIRCUIT DELAYS (4/5)

- Analyse the delay for the repeated block.



where X_i, Y_i are stable at 0t, while C_i is assumed to be stable at mt.

- Performing the delay calculation:

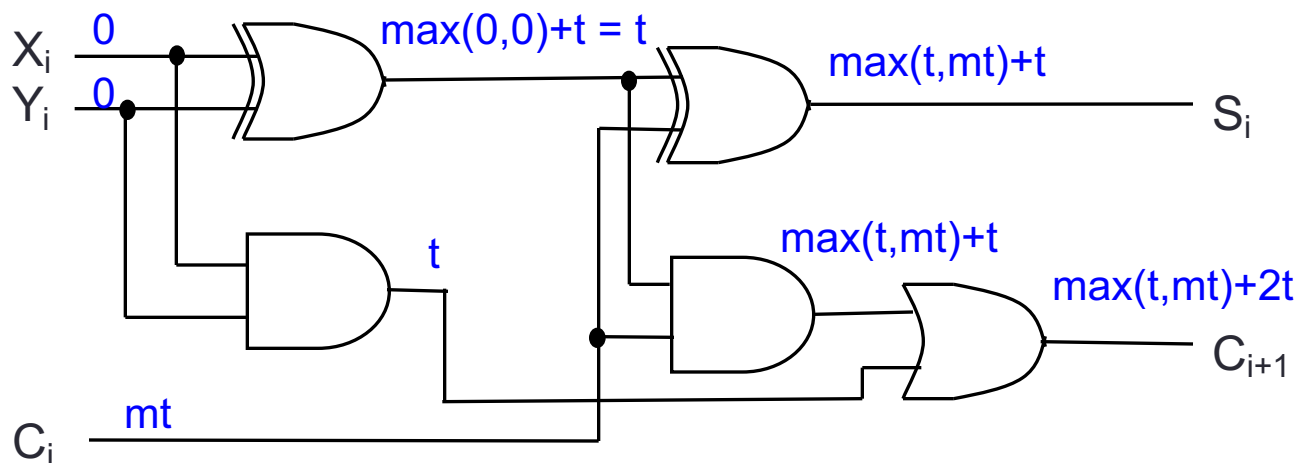

CIRCUIT DELAYS (5/5)

- Calculating:

When $i=1$, $m=0$; $S_1 = 2t$ and $C_2 = 3t$

When $i=2$, $m=3$; $S_2 = 4t$ and $C_3 = 5t$

When $i=3$, $m=5$; $S_3 = 6t$ and $C_4 = 7t$

When $i=4$, $m=7$; $S_4 = 8t$ and $C_5 = 9t$

- In general, an n -bit ripple-carry parallel adder will experience the following delay times:

$$S_n = ?$$

$$C_{n+1} = ?$$

- Propagation delay of ripple-carry parallel adders is proportional to the number of bits it handles.
- Maximum delay: ?

FASTER CIRCUITS


- Three ways of improving the speed of circuits:
 - Use better technology (eg. ECL faster than TTL gates) BUT
 - Faster technology is more expensive, needs more power, lower-level of integrations
 - Physical limits (eg. speed of light, size of atom)
 - Use gate-level designs to two-level circuits! (use sum-of-products/product-of-sums) BUT
 - Complicated designs for large circuits
 - Product/sum terms need MANY inputs!
 - Use clever look-ahead techniques BUT
 - There are additional costs (hopefully reasonable).

LOOK-AHEAD CARRY ADDER (1/6)

- Consider the FA, where intermediate signals are labelled as P_i and G_i :

$$P_i = X_i \oplus Y_i$$

$$G_i = X_i \cdot Y_i$$

 

- The outputs C_{i+1} , S_i , in terms of P_i , G_i , C_i are:

$$S_i = P_i \oplus C_i \quad \dots (1)$$

$$C_{i+1} = G_i + P_i \cdot C_i \quad \dots (2)$$

- Looking at equation (2):

$G_i = X_i \cdot Y_i$ is a *carry generate* signal, and

$P_i = X_i \oplus Y_i$ is a *carry propagate* signal.

LOOK-AHEAD CARRY ADDER (2/6)

- For 4-bit ripple-carry adder, the equations for the four carry signals are:


$$C_{i+1} = G_i + P_i \cdot C_i$$

$$C_{i+2} = G_{i+1} + P_{i+1} \cdot C_{i+1}$$

$$C_{i+3} = G_{i+2} + P_{i+2} \cdot C_{i+2}$$

$$C_{i+4} = G_{i+3} + P_{i+3} \cdot C_{i+3}$$

 - These formulae are deeply nested, as shown here for C_{i+2} :




4-level circuit for $C_{i+2} = G_{i+1} + P_{i+1} \cdot C_{i+1}$

LOOK-AHEAD CARRY ADDER (3/6)

- Nested formulae/gates cause more propagation delay.
- Reduce delay by expanding and flattening the formulae for carries. Example, for C_{i+2} :

$$\begin{aligned}C_{i+2} &= G_{i+1} + P_{i+1} \cdot C_{i+1} \\&= G_{i+1} + P_{i+1} \cdot (G_i + P_i \cdot C_i) \\&= G_{i+1} + P_{i+1} \cdot G_i + P_{i+1} \cdot P_i \cdot C_i\end{aligned}$$

- New faster circuit for C_{i+2} :

 

LOOK-AHEAD CARRY ADDER (4/6)


- Other carry signals can be similarly flattened:

$$\begin{aligned}
 C_{i+3} &= G_{i+2} + P_{i+2} \cdot C_{i+2} \\
 &= G_{i+2} + P_{i+2} \cdot (G_{i+1} + P_{i+1} \cdot G_i + P_{i+1} \cdot P_i \cdot C_i) \\
 &= G_{i+2} + P_{i+2} \cdot G_{i+1} + P_{i+2} \cdot P_{i+1} \cdot G_i + P_{i+2} \cdot P_{i+1} \cdot P_i \cdot C_i \\
 C_{i+4} &= G_{i+3} + P_{i+3} \cdot C_{i+3} \\
 &= G_{i+3} + P_{i+3} \cdot (G_{i+2} + P_{i+2} \cdot G_{i+1} + P_{i+2} \cdot P_{i+1} \cdot G_i + P_{i+2} \cdot P_{i+1} \cdot P_i \cdot C_i) \\
 &= G_{i+3} + P_{i+3} \cdot G_{i+2} + P_{i+3} \cdot P_{i+2} \cdot G_{i+1} + P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot G_i + \\
 &\quad P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot P_i \cdot C_i
 \end{aligned}$$

- Note that formulae gets longer with higher carries.
- Also, all carries are two-level sum-of-products expressions, in terms of the generate signals **G**s, the propagate signals **P**s, and the first carry-in **C_i**.


LOOK-AHEAD CARRY ADDER (5/6)

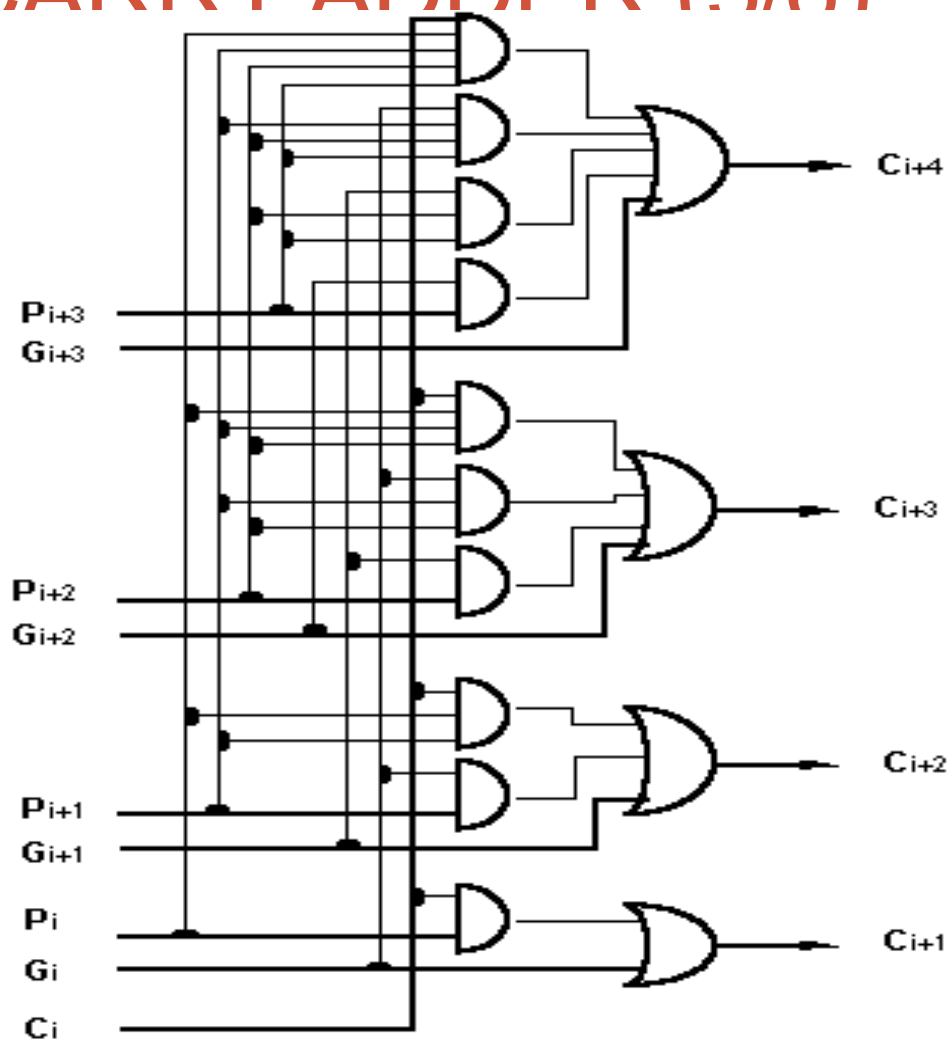- We employ look-ahead formula in this lookahead-carry adder circuit:



LOOK-AHEAD CARRY ADDER (6/6)

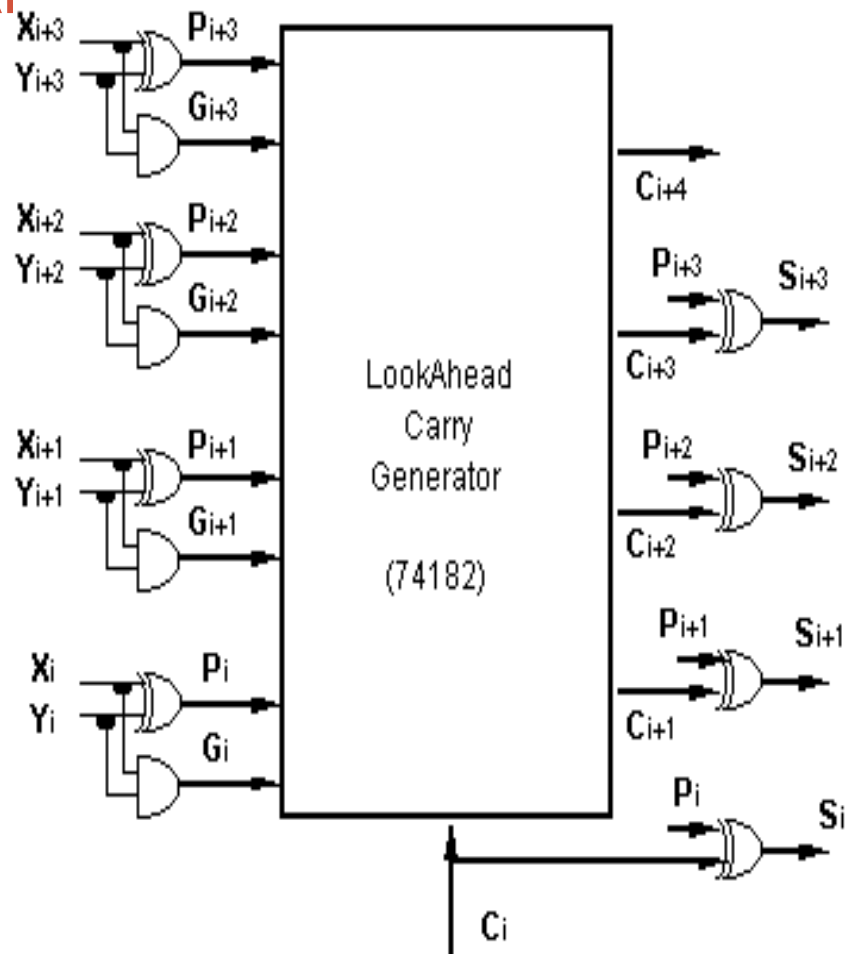- The 74182 IC chip allows faster lookahead adder to be built.
- Assuming gate delay is t , maximum propagation delay for circuit is hence $4t$
 - t to get generate and propagate signals
 - $2t$ to get the carries
 - t for the sum signals



4-Bit Adder with Look-Ahead

(74181)

QUICK REVIEW QUESTIONS

- DLD pages 128 - 129
Questions 6-1 to 6-4.



Q&A